 


A/D Converter and D/A Converter

• D/A Converters

- D/A converters convert digital signals into analog format.



Digital Data:

Evenly spaced discontinuous values

Temporally discrete, quantitatively discrete

Analog Data (Natural Phenomena):

Continuous range of values

Temporally continuous, quantitatively continuous

A/D Converter and D/A Converter

• A/D Converters

- An A/D converter is a device that converts analog signals (usually voltage) obtained from environmental (physical) phenomena into digital format
- Conversion involves a series of steps, including sampling, quantization, and coding.



A/D Converter and D/A Converter

A/D Converter Applications

Digital Audio:

Digital audio workstations, sound recording, pulse-code modulation

Digital signal processing:

TV tuner cards, microcontrollers, digital storage oscilloscopes

Scientific instruments:

Digital imaging systems, radar systems, temperature sensors

D/A Converter Applications

Digital Audio :

CD, MD, 1-bit Audio

Digital Video :

DVD, Digital Still Camera

Communication Equipment :


Smartphones, FAX, ADSI equipment

PCs :


Audio, video cards

Measurement instruments :


Programmable power supplies, etc.

 

Analogue and Digital Signals

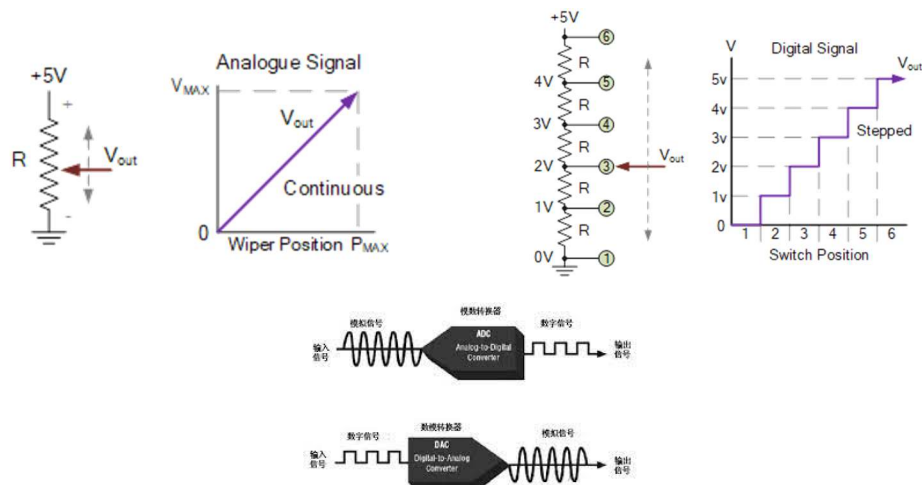

Analog to Digital (A/D) Converter

 


- Input signal
- Sampling rate
- Throughput
- Resolution
- Range
- Gain


Digital-to-Analog Conversion

- When data is in binary form, the 0's and 1's may be of several forms such as the TTL form where the logic zero may be a value up to 0.8 volts and the 1 may be a voltage from 2 to 5 volts. The data can be converted to clean digital form using gates which are designed to be on or off depending on the value of the incoming signal. Data in clean binary digital form can be converted to an analog form by using a summing amplifier. For example, a simple 4-bit D/A converter can be made with a four-input summing amplifier. More practical is the R-2R Network DAC.

Four-Bit D/A Converter

 

Inverting Summing Amplifier Circuit

 


$$I_F = I_1 + I_2 + I_3 + I_4 = \frac{V_{IN1}}{R_1} + \frac{V_{IN2}}{R_2} + \frac{V_{IN3}}{R_3} + \frac{V_{IN4}}{R_4}$$

$$V_{OUT} = \frac{R_F}{R_{IN}} \times V_{IN} = - \left(\frac{R_F}{R_1} V_{IN1} + \frac{R_F}{R_2} V_{IN2} + \frac{R_F}{R_3} V_{IN3} + \frac{R_F}{R_4} V_{IN4} \right)$$

$$\therefore V_{OUT} = - \frac{R_F}{R_{IN}} (V_{IN1} + V_{IN2} + V_{IN3} + V_{IN4})$$

Inverting Summing Amplifier Circuit

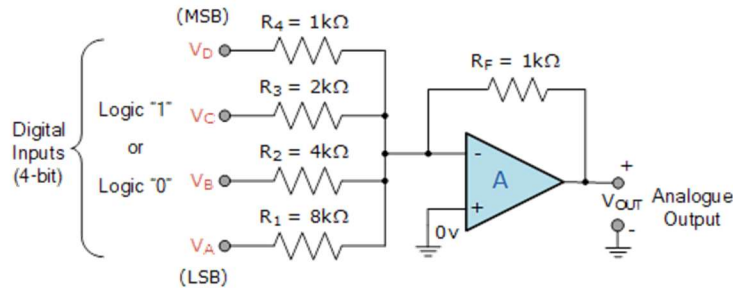


$$V_{OUT} = - \left[\frac{R_F}{R_4} V_D + \frac{R_F}{R_3} V_C + \frac{R_F}{R_2} V_B + \frac{R_F}{R_1} V_A \right]$$


$$V_{OUT} = - \left[\frac{1k\Omega}{1k\Omega} V_D + \frac{1k\Omega}{2k\Omega} V_C + \frac{1k\Omega}{4k\Omega} V_B + \frac{1k\Omega}{8k\Omega} V_A \right]$$

$$V_{OUT} = - \left[1V_D + \frac{1}{2}V_C + \frac{1}{4}V_B + \frac{1}{8}V_A \right]$$


4-bit R-2R Resistive Ladder Network

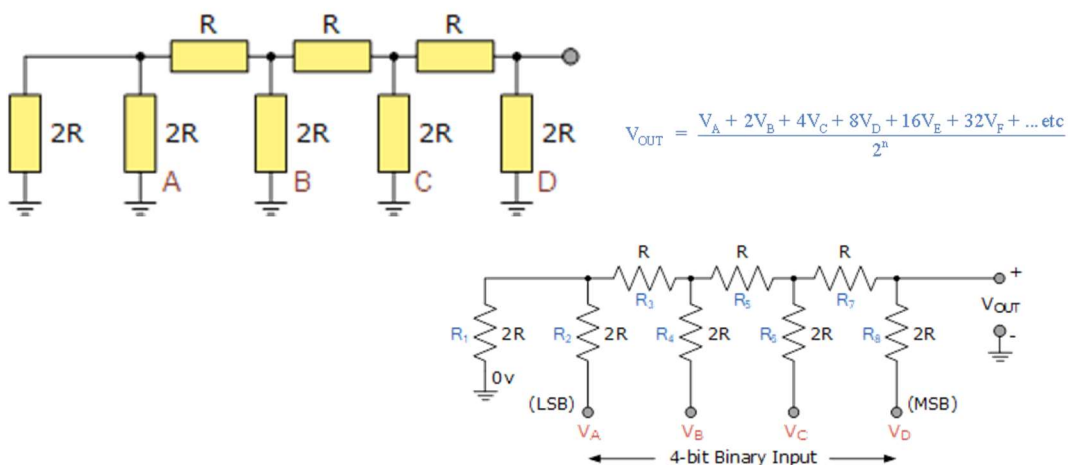


4-bit R-2R Resistive Ladder Network

 

4-bit R-2R Resistive Ladder Network

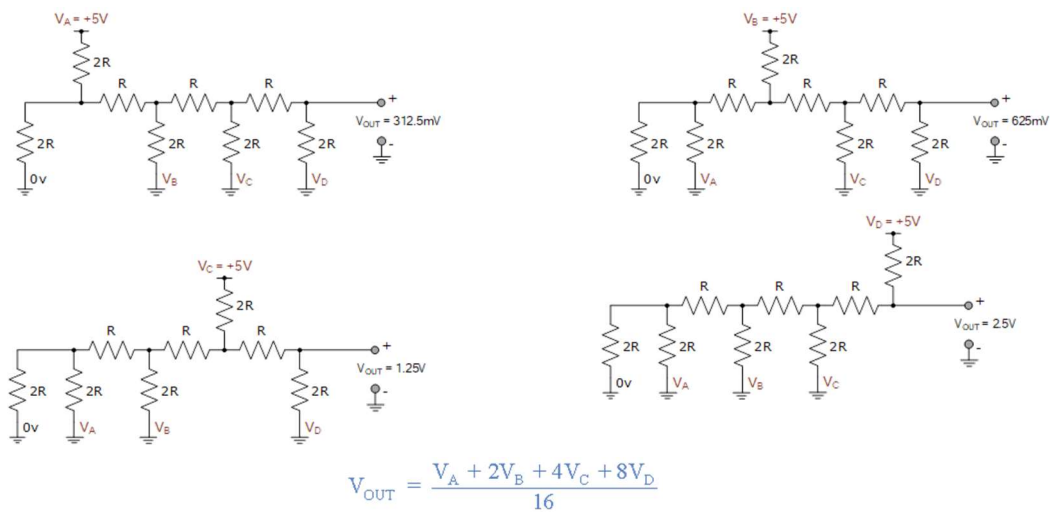


R-2R Ladder DAC

 


$$V_{out} = \frac{R_f}{R} V_{ref} \left[\frac{D_0}{16} + \frac{D_1}{8} + \frac{D_2}{4} + \frac{D_3}{2} \right]$$



R-2R Ladder DAC Details

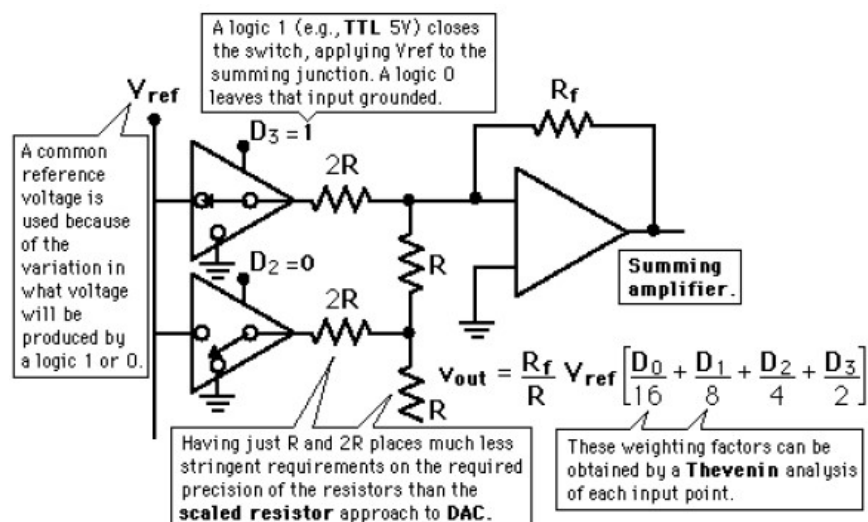

Thevenin Example: R-2R Ladder

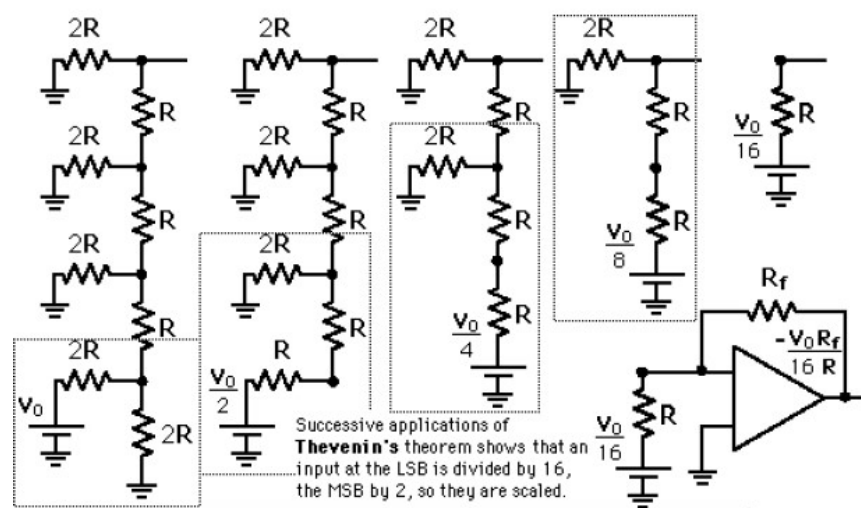

4-bit Binary Counting R-2R DAC

 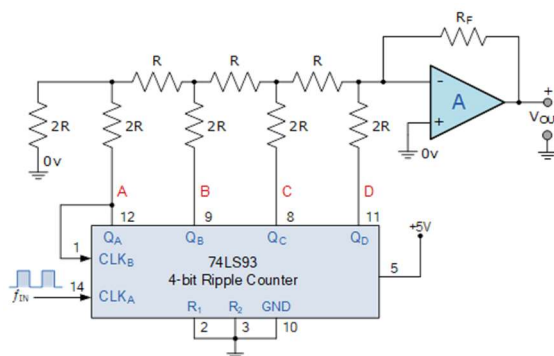

Base 10 number	SCALE	+ 10V FS	BANARY	GRAY
+15	+FS - 1LSB = +15/16 FS	9.375	1 1 1 1	1 0 0 0
+14	+7/8 FS	8.750	1 1 1 0	1 0 0 1
+13	+13/16 FS	8.125	1 1 0 1	1 0 1 1
+12	+3/4 FS	7.500	1 1 0 0	1 0 1 0
+11	+11/16 FS	6.875	1 0 1 1	1 1 1 0
+10	+5/8 FS	6.250	1 0 1 0	1 1 1 1
+9	+9/16 FS	5.625	1 0 0 1	1 1 0 1
+8	+1/2 FS	5.000	1 0 0 0	1 1 0 0
+7	+7/16 FS	4.375	0 1 1 1	0 1 0 0
+6	+3/8 FS	3.750	0 1 1 0	0 1 0 1
+5	+5/16 FS	3.125	0 1 0 1	0 1 1 1
+4	+1/4 FS	2.500	0 1 0 0	0 1 1 0
+3	+3/16 FS	1.875	0 0 1 1	0 0 1 0
+2	+1/8 FS	1.250	0 0 1 0	0 0 1 1
+1	1LSB = +1/16 FS	0.625	0 0 0 1	0 0 0 1
0	0	0.000	0 0 0 0	0 0 0 0

Bipolar Codes

Base 10 number	SCALE	± 5V FS	OFFSET BINARY	TWOS COMP.	ONES COMP.	SIGN MAG.
+7	+FS - 1LSB = +7/8 FS	+4.375	1 1 1 1	0 1 1 1	0 1 1 1	0 1 1 1
+6	+3/4 FS	+3.750	1 1 1 0	0 1 1 0	0 1 1 0	0 1 1 0
+5	+5/8 FS	+3.125	1 1 0 1	0 1 0 1	0 1 0 1	0 1 0 1
+4	+1/2 FS	+2.500	1 1 0 0	0 1 0 0	0 1 0 0	0 1 0 0
+3	+3/8 FS	+1.875	1 0 1 1	0 0 1 1	0 0 1 1	0 0 1 1
+2	+1/4 FS	+1.250	1 0 1 0	0 0 1 0	0 0 1 0	0 0 1 0
+1	+1/8 FS	+0.625	1 0 0 1	0 0 0 1	0 0 0 1	0 0 0 1
0	0	0.000	1 0 0 0	0 0 0 0	*0 0 0 0	*1 0 0 0
-1	-1/8 FS	-0.625	0 1 1 1	1 1 1 1	1 1 1 0	1 0 0 1
-2	-1/4 FS	-1.250	0 1 1 0	1 1 1 0	1 1 0 1	1 0 1 0
-3	-3/8 FS	-1.875	0 1 0 1	1 1 0 1	1 1 0 0	1 0 1 1
-4	-1/2 FS	-2.500	0 1 0 0	1 1 0 0	1 0 1 1	1 1 0 0
-5	-5/8 FS	-3.125	0 0 1 1	1 0 1 1	1 0 1 0	1 1 0 1
-6	-3/4 FS	-3.750	0 0 1 0	1 0 1 0	1 0 0 1	1 1 1 0
-7	-FS + 1LSB = -7/8 FS	-4.375	0 0 0 1	1 0 0 1	1 0 0 0	1 1 1 1
-8	+FS	-5.000	0 0 0 0	1 0 0 0		
NOT NORMALLY USED IN COMPUTATIONS					ONES COMP.	TWOS COMP.
				0+	0 0 0 0	1 0 0 0
				0-	1 1 1 1	1 0 0 0

Quantization: The Size of a Least Significant Bit (LSB)


Resolution N	2 ^N	VOLTAGE (10V FS)	ppm FS	% FS	dB FS
2-bit	4	2.5V	250.000	25	-12
4-bit	16	625mV	62.500	6.25	-24
6-bit	64	156mV	15.625	1.56	-36
8-bit	256	39.1mV	3.906	0.39	-48
10-bit	1.024	9.77mV (10mV)	977	0.098	-60
12-bit	4.096	2.44mV	244	0.024	-72
14-bit	16.384	610μV	61	0.0061	-84
16-bit	65.536	153μV	15	0.0015	-96
18-bit	262.144	38μV	4	0.0004	-108
20-bit	1.048.576	9.54μV (10μV)	1	0.001	-120
22-bit	4.194.304	2.38μV	0.24	0.000024	-132
24-bit	16.777.216	596nV*	0.06	0.000006	-144

The resolution of data converters

$$1 \text{ LSB} = \frac{FSR}{(2^n - 1)} \text{ for } n\text{-bit converter}$$


The Ideal Transfer Function (ADC)

 The theoretical ideal transfer function for an ADC is a straight line, however, the practical ideal transfer function is a uniform staircase characteristic shown in Figure .





The Ideal Transfer Function (DAC)

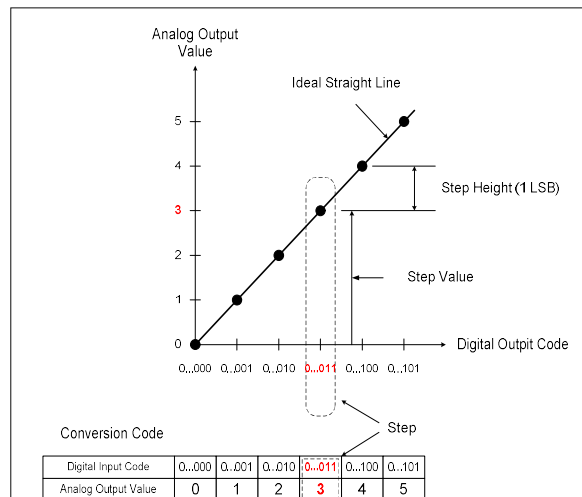The DAC theoretical ideal transfer function would also be a straight line with an infinite number of steps but practically it is a series of points that fall on the ideal straight line as shown in Figure




Analogue to Digital Converter

  
- Analogue to Digital Converter, or ADC, is a data converter which allows digital circuits to interface with the real world by encoding an analogue signal into a binary code




Comparator Circuit

 

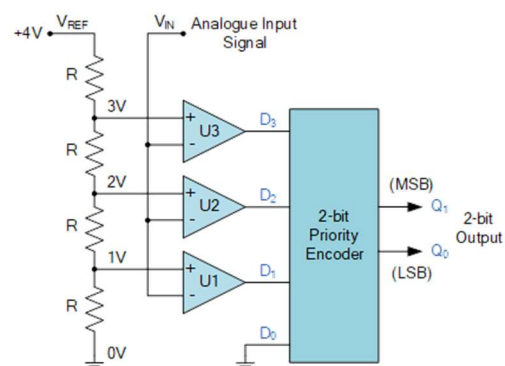2-bit Analogue to Digital Converter Circuit




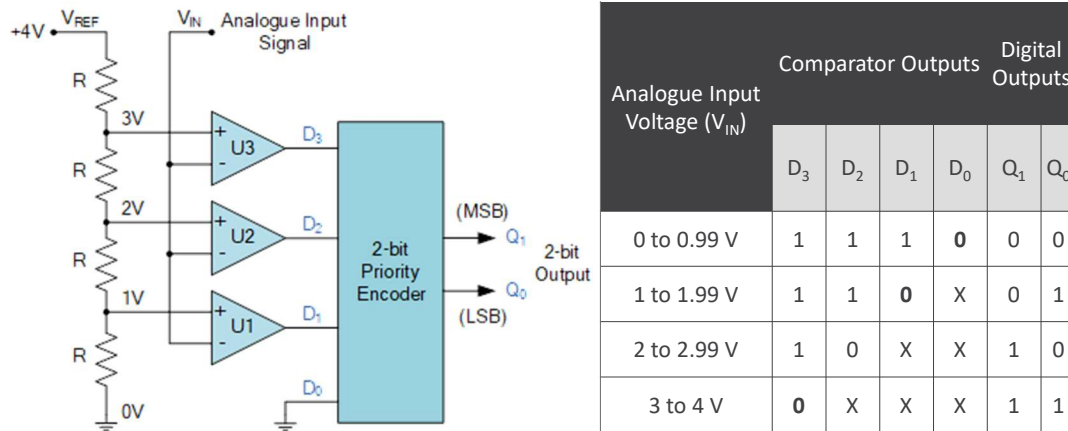2-bit Analogue to Digital Converter Circuit




Where: "X" is a "don't care", that is either a logic "0" or a logic "1" condition.

2-bit ADC Using Diodes

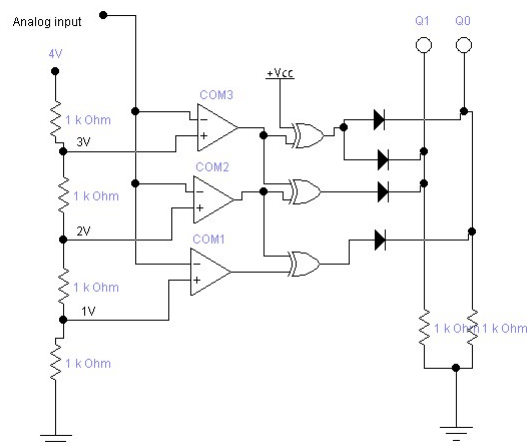


 3-bit Analogue to Digital Converter Circuit




Analogue Input Voltage (V _{IN})	Comparator Outputs								Digital Outputs		
	D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	Q ₂	Q ₁	Q ₀
0 to 0.49 V	1	1	1	1	1	1	1	0	0	0	0
0.5 to 0.99 V	1	1	1	1	1	1	0	X	0	0	1
1.0 to 1.49 V	1	1	1	1	1	0	X	X	0	1	0
1.5 to 1.99 V	1	1	1	1	0	X	X	X	0	1	1
2.0 to 2.49 V	1	1	1	0	X	X	X	X	1	0	0
2.5 to 2.99 V	1	1	0	X	X	X	X	X	1	0	1
3.0 to 3.49 V	1	0	X	X	X	X	X	X	1	1	0
3.5 to 4.0 V	0	X	X	X	X	X	X	X	1	1	1

Digital Ramp ADC

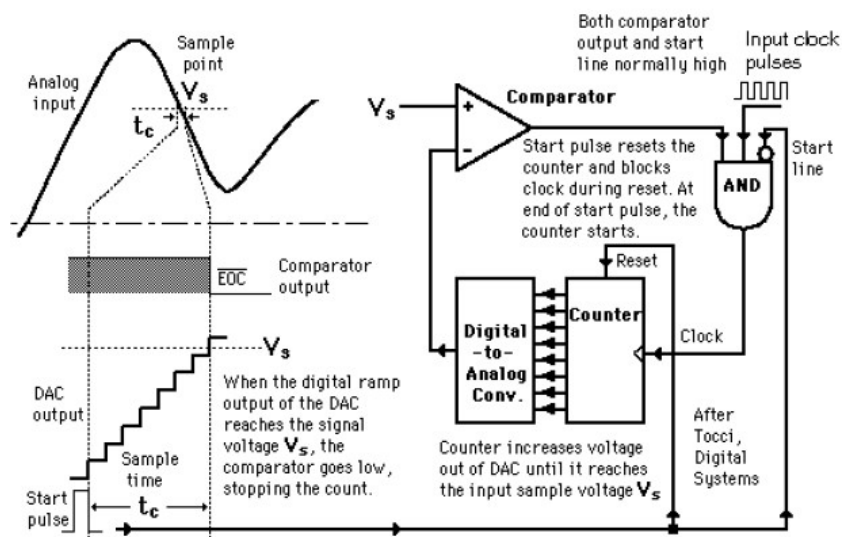


Successive Approximation ADC

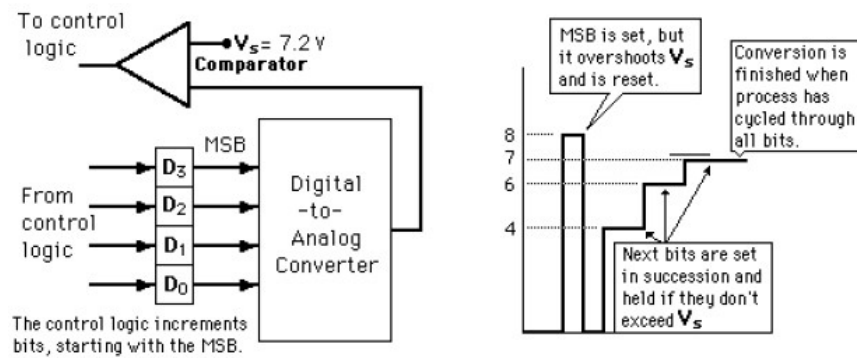


Successive Approximation ADC

- The successive approximation ADC is much faster than the digital ramp ADC because it uses digital logic to converge on the value closest to the input voltage. A [comparator](#) and a [DAC](#) are used in the process.

Successive Approximation ADC

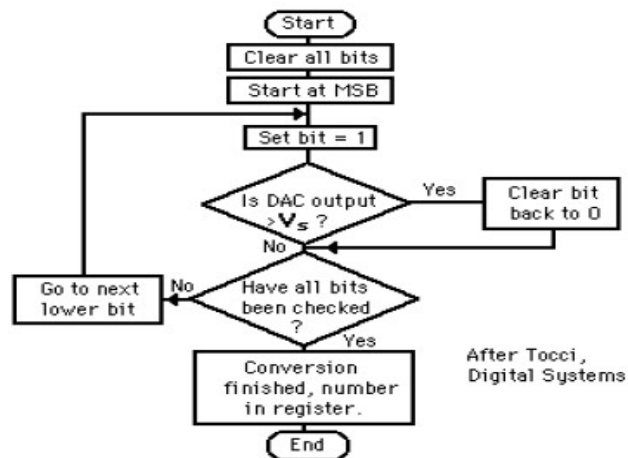


Successive-approximation ADC

 


DAC = digital-to-analog converter
 EOC = end of conversion
 SAR = successive approximation register
 S/H = sample and hold circuit
 V_{IN} = input voltage
 V_{REF} = reference voltage

Successive-approximation ADC

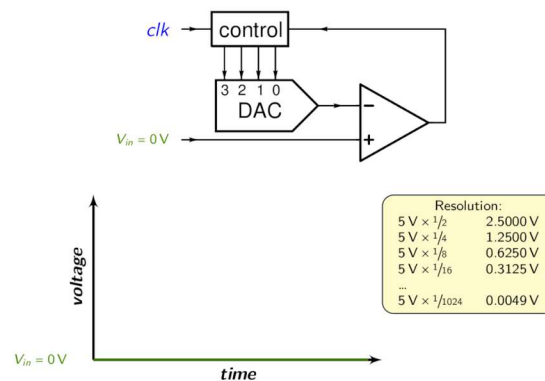Successive Approximation – example of a 4-bit ADC



Flash ADC

 

Illustrated is a 3-bit flash ADC with resolution 1 volt (after Tocci). The resistor net and [comparators](#) provide an input to the combinational logic circuit, so the conversion time is just the propagation delay through the network - it is not limited by the clock rate or some convergence sequence. It is the fastest type of ADC available, but requires a comparator for each value of output (63 for 6-bit, 255 for 8-bit, etc.) Such ADCs are available in IC form up to 8-bit and 10-bit flash ADCs (1023 comparators) are planned. The encoder logic executes a truth table to convert the ladder of inputs to the binary number output.

Characteristics ADC

SYSTEM ARCHITECTURE	RESOLUTION	SPEED	ADVANTAGE / DRAWBACKS
Flash	8 bits	250MSPS – 1GSPS	+ Extremely fast + High input bandwidth - Higher power consumption - Large die size - High input capacitance - Expansive - Sparkle codes
SAR	10 bits – 16 bits	76kSPS – 250kSPS	+ High resolution and accuracy + Low power consumption + Few external components - Low input bandwidth - Limited sampling rate - V_{IN} must retain constant during conv.
Integrating	> 18 bits	< 50 kSPS	+ High resolution + Low supply current + Excellent noise rejection - Low speed
Sigma-Delta ($\Sigma-\Delta$)	> 16 bits	> 200 kSPS	+ High resolution + High input bandwidth + Digital on-chip filtering - External T/H - Limited sampling rate
Pipeline	12 bits – 16 bits	1MSPS – 80MSPS	+ High throughput rate + Low power consumption + Digital error correction and on-chip self-calibration - Required duty-cycle typical - Required minimum clock frequency