
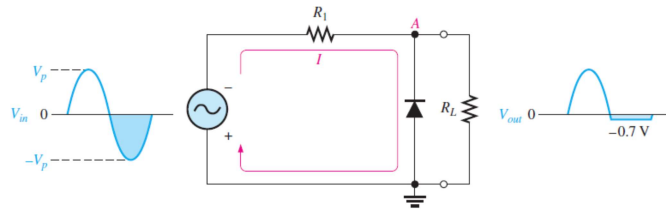


DIODE LIMITERS AND CLAMPERS


Diode Limiters

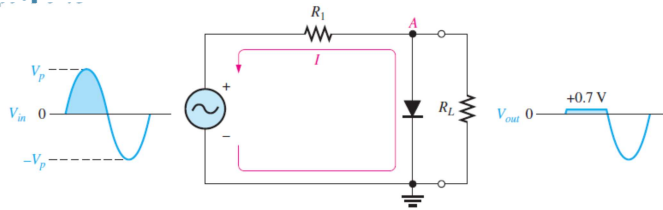

$$V_{out} = \left(\frac{R_L}{R_1 + R_L} \right) V_{in}$$

DIODE LIMITERS AND CLAMPERS

Diode Limiters

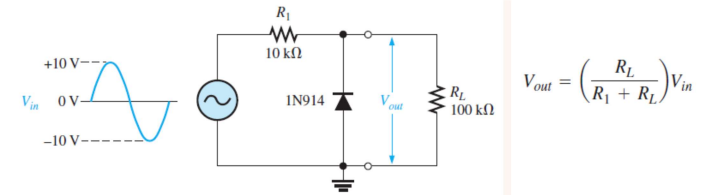


$$V_{out} = \left(\frac{R_L}{R_1 + R_L} \right) V_{in}$$

The diode is forward-biased and conducts when the input voltage goes below -0.7 V. So, for the negative limiter, determine the peak output voltage across R_L by the following equation:



$$V_{p(out)} = \left(\frac{R_L}{R_1 + R_L} \right) V_{p(in)} = \left(\frac{100 \text{ k}\Omega}{110 \text{ k}\Omega} \right) 10 \text{ V} = 9.09 \text{ V}$$

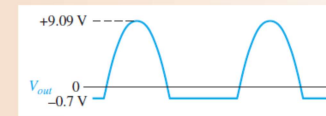The scope will display an output waveform as shown in Figure 2-54.




DIODE LIMITERS AND CLAMPERS

Biased Limiters

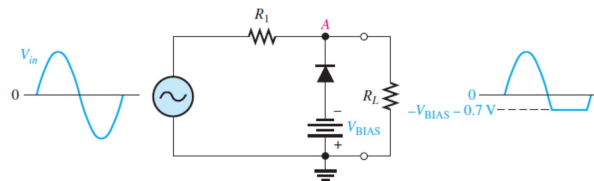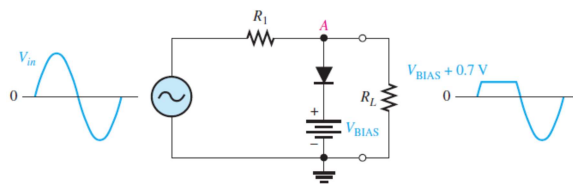


DIODE LIMITERS AND CLAMPERS

Biased Limiters

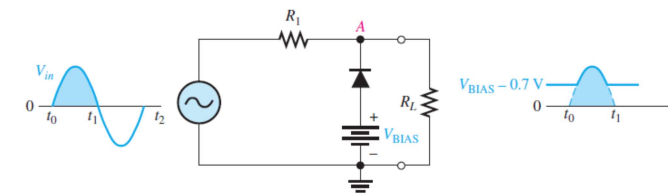


(a)

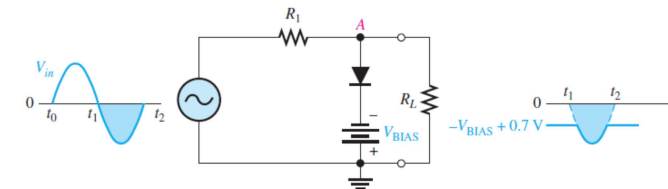

DIODE LIMITERS AND CLAMPERS

Biased Limiters


Figure 2-58 shows a circuit combining a positive limiter with a negative limiter. Determine the output voltage waveform.

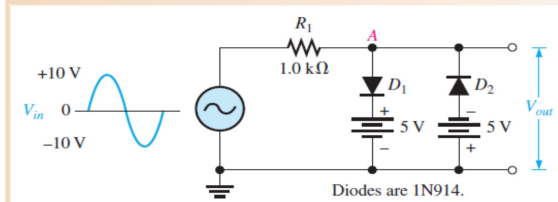

When the voltage at point A reaches +5.7 V, diode D_1 conducts and limits the waveform to +5.7 V. Diode D_2 does not conduct until the voltage reaches -5.7 V. Therefore, positive voltages above +5.7 V and negative voltages below -5.7 V are clipped off. The resulting output voltage waveform is shown in Figure 2-59.


FIGURE 2-59

Output voltage waveform for Figure 2-58.

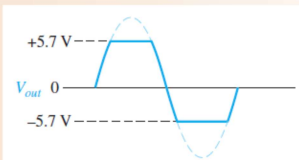

DIODE LIMITERS AND CLAMPERS



Diode Clampers

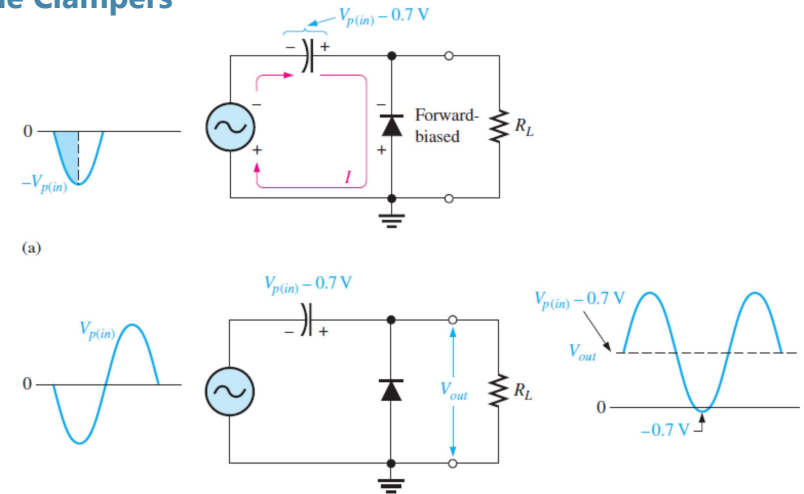

Special-Purpose Diodes

THE ZENER DIODE

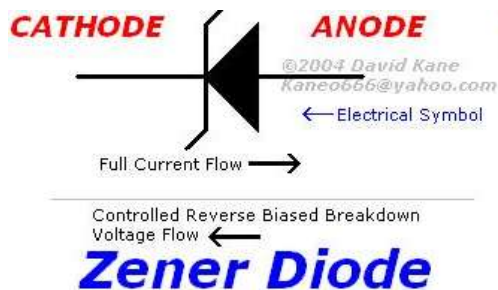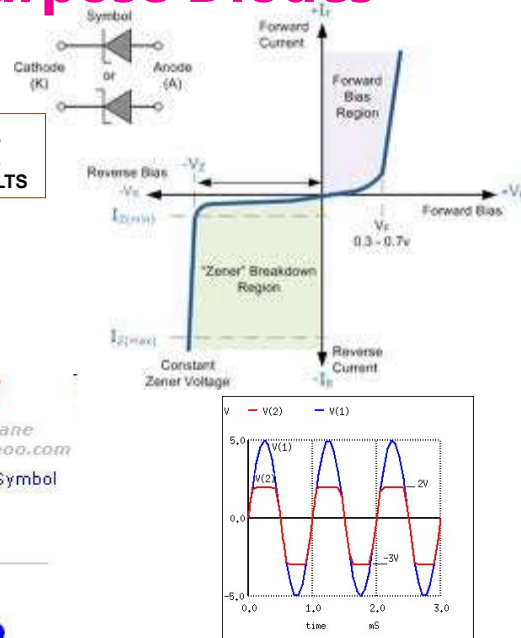
WORK AT SPECIFIC BREAKDOWN VOLTAGE. FUNCTION AS A VOLTAGE SENSITIVE SWITCH. THIS VOLTAGE (V_Z) VARY FROM 2 TO 200 VOLTS



THE ZENER DIODE

FIGURE 3-3

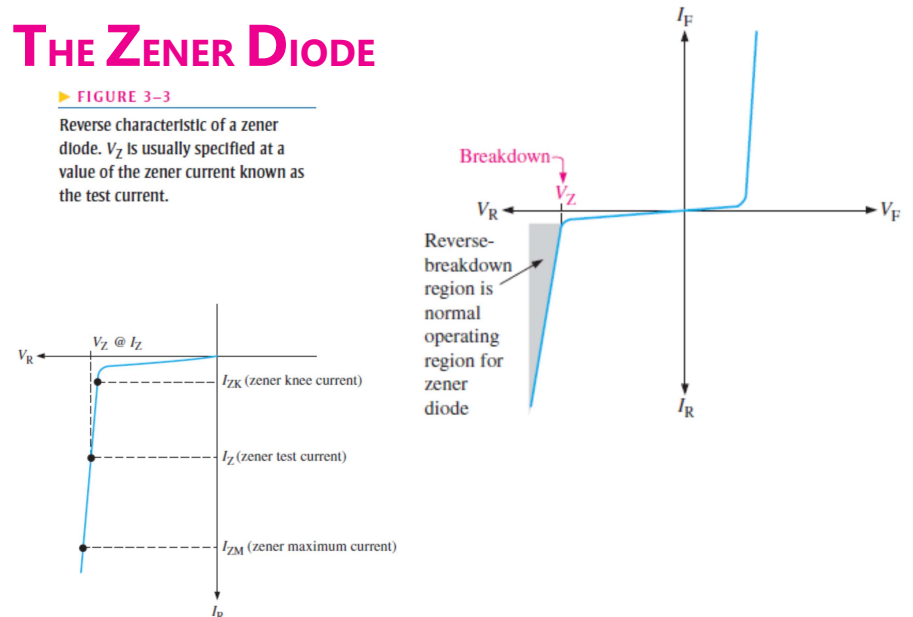Reverse characteristic of a zener diode. V_Z is usually specified at a value of the zener current known as the test current.




Special-Purpose Diodes


THE ZENER DIODE

zener impedance (resistance), Z_Z

$$Z_Z = \frac{\Delta V_Z}{\Delta I_Z}$$

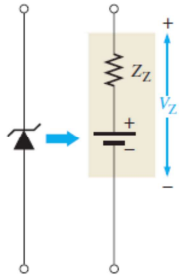

(a) Practical model

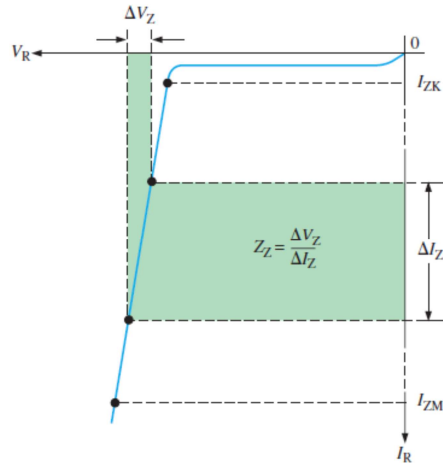

(b) Characteristic curve. The slope is exaggerated for illustration.

Special-Purpose Diodes

THE ZENER DIODE

$$\Delta V_Z = V_Z \times TC \times \Delta T$$

zener impedance (resistance), Z_Z

$$Z_Z = \frac{\Delta V_Z}{\Delta I_Z}$$

An 8.2 V zener diode (8.2 V at 25°C) has a positive temperature coefficient of 0.05%/°C. What is the zener voltage at 60°C?

The change in zener voltage is

$$\begin{aligned} \Delta V_Z &= V_Z \times TC \times \Delta T = (8.2 \text{ V})(0.05\%/^{\circ}\text{C})(60^{\circ}\text{C} - 25^{\circ}\text{C}) \\ &= (8.2 \text{ V})(0.0005/^{\circ}\text{C})(35^{\circ}\text{C}) = 144 \text{ mV} \end{aligned}$$

Notice that 0.05%/°C was converted to 0.0005/°C. The zener voltage at 60°C is

$$V_Z + \Delta V_Z = 8.2 \text{ V} + 144 \text{ mV} = 8.34 \text{ V}$$

Special-Purpose Diodes

THE ZENER DIODE

zener impedance (resistance), Z_Z

$$Z_Z = \frac{\Delta V_Z}{\Delta I_Z}$$

$$\Delta V_Z = V_Z \times TC \times \Delta T$$

$$P_D = V_Z I_Z$$

$$P_{D(\text{derated})} = P_{D(\text{max})} - (\text{mW}/^{\circ}\text{C})\Delta T$$

A certain zener diode has a maximum power rating of 400 mW at 50°C and a derating factor of 3.2 mW/°C. Determine the maximum power the zener can dissipate at a temperature of 90°C.

$$\begin{aligned} P_{D(\text{derated})} &= P_{D(\text{max})} - (\text{mW}/^{\circ}\text{C})\Delta T \\ &= 400 \text{ mW} - (3.2 \text{ mW}/^{\circ}\text{C})(90^{\circ}\text{C} - 50^{\circ}\text{C}) \\ &= 400 \text{ mW} - 128 \text{ mW} = 272 \text{ mW} \end{aligned}$$

A certain 50 W zener diode must be derated with a derating factor of 0.5 W/°C above 75°C. Determine the maximum power it can dissipate at 160°C.

Special-Purpose Diodes

THE ZENER DIODE

FAIRCHILD
SEMICONDUCTOR®

1N4728A - 1N4764A

Zeners



DO-41 Glass case
COLOR BAND DENOTES CATHODE

Absolute Maximum Ratings * $T_A = 25^{\circ}\text{C}$ unless otherwise noted

Symbol	Parameter	Value	Units
P_D	Power Dissipation @ $T_L \leq 50^{\circ}\text{C}$, Lead Length = 3/8"	1.0	W
	Derate above 50°C	6.67	mW/°C
T_J, T_{STG}	Operating and Storage Temperature Range	-65 to +200	°C

*These ratings are limiting values above which the serviceability of the diode may be impaired.

Special-Purpose Diodes

THE ZENER DIODE


Electrical Characteristics $T_A = 25^\circ\text{C}$ unless otherwise noted

Device	V_Z (V) @ I_Z (Note 1)			Test Current I_Z (mA)	Max. Zener Impedance			Leakage Current	
	Min.	Typ.	Max.		Z_Z @ I_Z (Ω)	Z_{ZK} @ I_{ZK} (Ω)	I_{ZK} (mA)	I_R (μA)	V_R (V)
1N4728A	3.315	3.3	3.465	76	10	400	1	100	1
1N4729A	3.42	3.6	3.78	69	10	400	1	100	1
1N4730A	3.705	3.9	4.095	64	9	400	1	50	1
1N4731A	4.085	4.3	4.515	58	9	400	1	10	1
1N4732A	4.465	4.7	4.935	53	8	500	1	10	1
1N4733A	4.845	5.1	5.355	49	7	550	1	10	1
1N4734A	5.32	5.6	5.88	45	5	600	1	10	2
1N4735A	5.89	6.2	6.51	41	2	700	1	10	3
1N4736A	6.46	6.8	7.14	37	3.5	700	1	10	4
1N4737A	7.125	7.5	7.875	34	4	700	0.5	10	5
1N4738A	7.79	8.2	8.61	31	4.5	700	0.5	10	6
1N4739A	8.645	9.1	9.555	28	5	700	0.5	10	7
1N4740A	9.5	10	10.5	25	7	700	0.25	10	7.6
1N4741A	10.45	11	11.55	23	8	700	0.25	5	8.4
1N4742A	11.4	12	12.6	21	9	700	0.25	5	9.1
1N4743A	12.35	13	13.65	19	10	700	0.25	5	9.9
1N4744A	14.25	15	15.75	17	14	700	0.25	5	11.4
1N4745A	15.2	16	16.8	15.5	16	700	0.25	5	12.2
1N4746A	17.1	18	18.9	14	20	750	0.25	5	13.7
1N4747A	19	20	21	12.5	22	750	0.25	5	15.2

Special-Purpose Diodes

THE ZENER DIODE

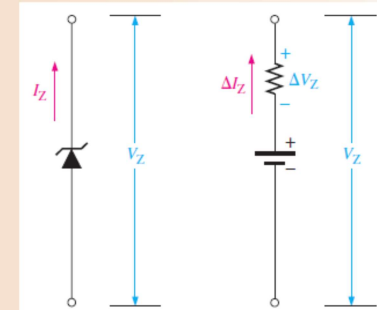From the datasheet in Figure 3-7, a 1N4736A zener diode has a Z_Z of $3.5\ \Omega$. The datasheet gives $V_Z = 6.8\ \text{V}$ at a test current, I_Z , of $37\ \text{mA}$. What is the voltage across the zener terminals when the current is $50\ \text{mA}$? When the current is $25\ \text{mA}$? Figure 3-8 represents the zener diode.



Special-Purpose Diodes

THE ZENER DIODE

For $I_Z = 50\ \text{mA}$: The $50\ \text{mA}$ current is a $13\ \text{mA}$ increase above the test current, I_Z , of $37\ \text{mA}$.

$$\Delta I_Z = I_Z - 37\ \text{mA} = 50\ \text{mA} - 37\ \text{mA} = +13\ \text{mA}$$

$$\Delta V_Z = \Delta I_Z Z_Z = (13\ \text{mA})(3.5\ \Omega) = +45.5\ \text{mV}$$

The change in voltage due to the increase in current above the I_Z value causes the zener terminal voltage to increase. The zener voltage for $I_Z = 50\ \text{mA}$ is

$$V_Z = 6.8\ \text{V} + \Delta V_Z = 6.8\ \text{V} + 45.5\ \text{mV} = \mathbf{6.85\ \text{V}}$$

For $I_Z = 25\ \text{mA}$: The $25\ \text{mA}$ current is a $12\ \text{mA}$ decrease below the test current, I_Z , of $37\ \text{mA}$.

$$\Delta I_Z = -12\ \text{mA}$$


$$\Delta V_Z = \Delta I_Z Z_Z = (-12\ \text{mA})(3.5\ \Omega) = -42\ \text{mV}$$

The change in voltage due to the decrease in current below the test current causes the zener terminal voltage to decrease. The zener voltage for $I_Z = 25\ \text{mA}$ is


$$V_Z = 6.8\ \text{V} - \Delta V_Z = 6.8\ \text{V} - 42\ \text{mV} = \mathbf{6.76\ \text{V}}$$

Special-Purpose Diodes

THE ZENER DIODE Application

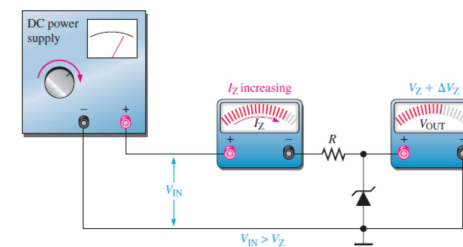

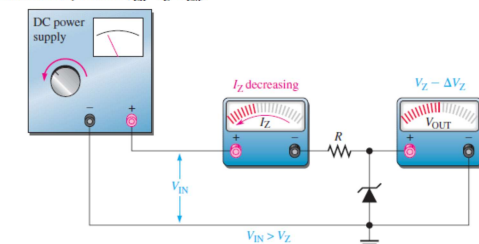(a) As the input voltage increases, the output voltage remains nearly constant ($I_{ZK} < I_Z < I_{ZM}$).




(b) As the input voltage decreases, the output voltage remains nearly constant ($I_{ZK} < I_Z < I_{ZM}$).

Special-Purpose Diodes

THE ZENER DIODE Application

Determine the minimum and the maximum input voltages that can be regulated by the zener diode in Figure 3–11.


► FIGURE 3–11

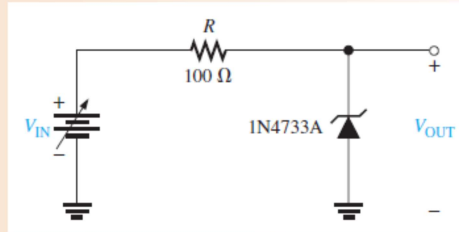

From the datasheet in Figure 3–7 for the 1N4733A: $V_Z = 5.1 \text{ V}$ at $I_Z = 49 \text{ mA}$, $I_{ZK} = 1 \text{ mA}$, and $Z_Z = 7 \Omega$ at I_Z . For simplicity, assume this value of Z_Z over the range of current values. The equivalent circuit is shown in Figure 3–12.

Special-Purpose Diodes

THE ZENER DIODE Application

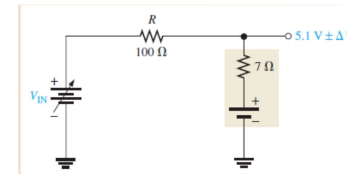

At $I_{ZK} = 1 \text{ mA}$, the output voltage is

$$V_{OUT} \cong 5.1 \text{ V} + \Delta V_Z = 5.1 \text{ V} - (I_Z - I_{ZK})Z_Z = 5.1 \text{ V} - (49 \text{ mA} - 1 \text{ mA})(7 \Omega) = 5.1 \text{ V} - (48 \text{ mA})(7 \Omega) = 5.1 \text{ V} - 0.336 \text{ V} = 4.76 \text{ V}$$

Therefore,

$$V_{IN(\min)} = I_{ZK}R + V_{OUT} = (1 \text{ mA})(100 \Omega) + 4.76 \text{ V} = 4.86 \text{ V}$$

To find the maximum input voltage, first calculate the maximum zener current. Assume the temperature is 50°C or below; so from Figure 3–7, the power dissipation is 1 W .

$$I_{ZM} = \frac{P_{D(\max)}}{V_Z} = \frac{1 \text{ W}}{5.1 \text{ V}} = 196 \text{ mA}$$

At I_{ZM} , the output voltage is

$$V_{OUT} \cong 5.1 \text{ V} + \Delta V_Z = 5.1 \text{ V} + (I_{ZM} - I_Z)Z_Z = 5.1 \text{ V} + (147 \text{ mA})(7 \Omega) = 5.1 \text{ V} + 1.03 \text{ V} = 6.13 \text{ V}$$


Therefore,

$$V_{IN(\max)} = I_{ZM}R + V_{OUT} = (196 \text{ mA})(100 \Omega) + 6.13 \text{ V} = 25.7 \text{ V}$$

Special-Purpose Diodes

THE ZENER DIODE Application

Zener Limiter

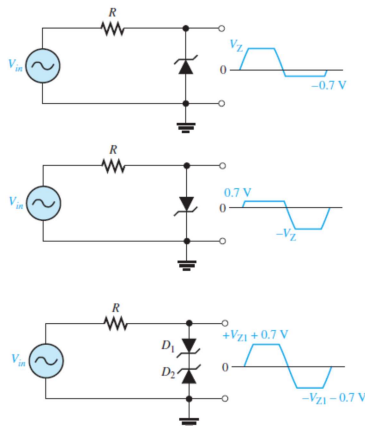


Special-Purpose Diodes

VARACTOR DIODE


► FIGURE 3–21

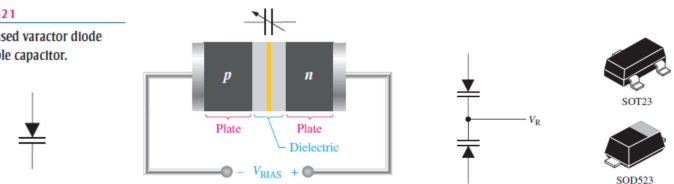The reverse-biased varactor diode acts as a variable capacitor.



Basic Operation

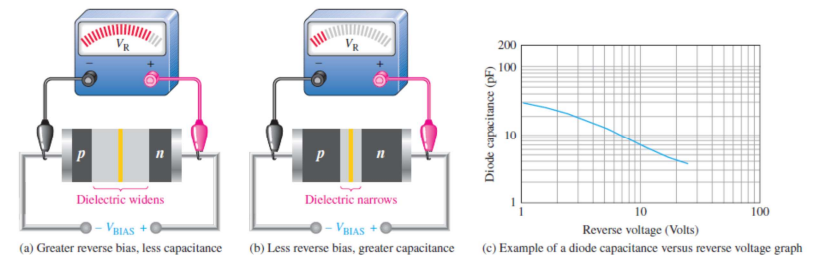Recall that capacitance is determined by the parameters of plate area (A), dielectric constant (ϵ), and plate separation (d), as expressed in the following formula:



Special-Purpose Diodes

VARIATOR DIODE


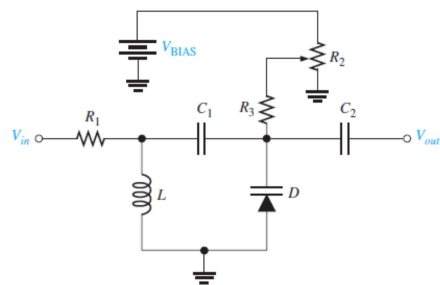
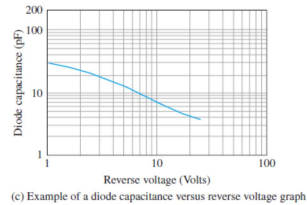
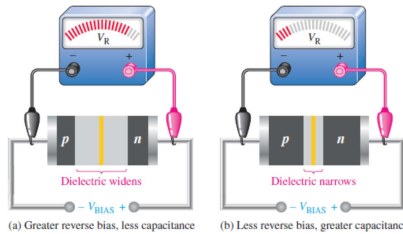
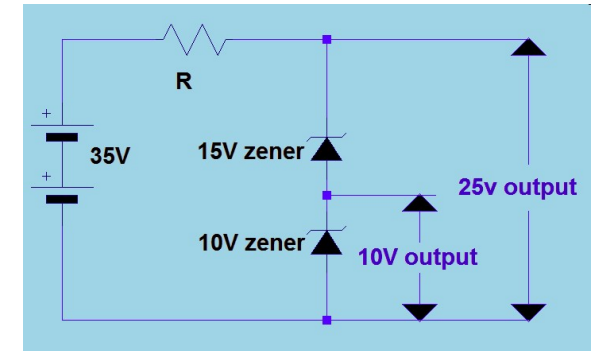




FIGURE 3-26
A resonant band-pass filter using a varactor diode for adjusting the resonant frequency over a specified range.

$$f_r \cong \frac{1}{2\pi\sqrt{LC}}$$

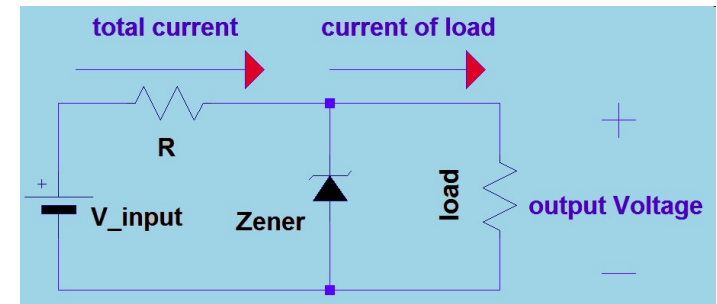


LIGHT EMITTING DIODE (LED)

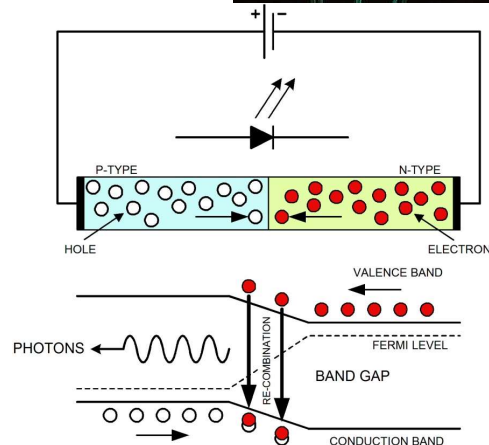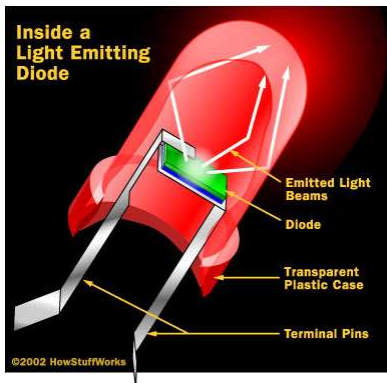ALL DIODES EMIT SOME EM RADIATION WHEN FORWARD BIASED. DIODES MADE FROM CERTAIN SEMICONDUCTORS EMIT LOTS OF LIGHT. THESE ARE CALLED LEDS



LED: The Inside View

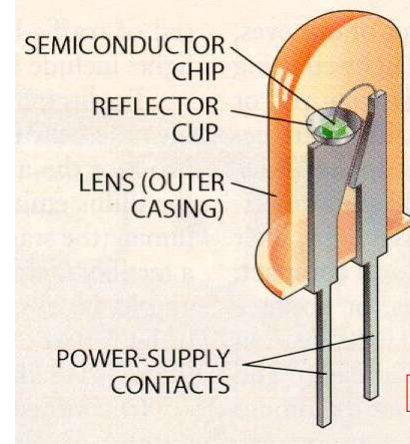


LEDS CAN EMIT AND DETECT LIGHT

YOU TUBE: MAKE presents: The LED <http://www.youtube.com/watch?v=P3PDLsJQcGI>

PN JUNCTION LIGHT DETECTORS (PHOTODIODES)

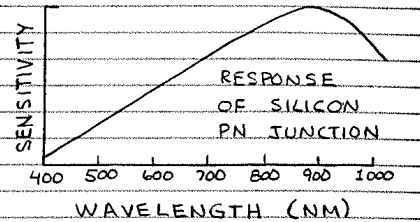
PN JUNCTION LIGHT DETECTORS FORM THE LARGEST FAMILY OF PHOTONIC SEMICONDUCTORS. MOST ARE MADE FROM SILICON AND CAN DETECT BOTH VISIBLE LIGHT AND NEAR-INFRARED.




PHOTODIODES

ARE DESIGNED TO DETECT LIGHT. (ALL PN JUNCTIONS ARE LIGHT SENSITIVE) THEY HAVE A WINDOW WHERE LIGHT ENTERS TO A LARGE EXPOSED JUNCTION REGION. SOME COMMON USES INCLUDE CAMERAS, ALARMS, LIGHTWAVE DIODES (LASERS).

PHOTODIODE SYMBOL

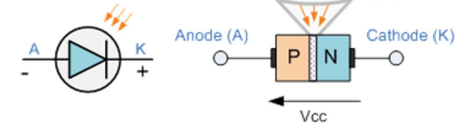

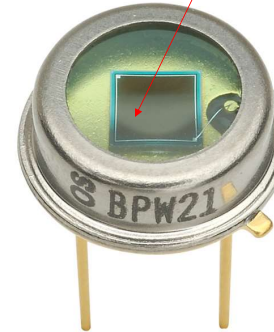
PHOTODIODES CAN BE USED TO DETECT FAST PULSES OF INFRARED LIGHT, USED IN LIGHTWAVE COMMUNICATIONS



how photodiode works <http://www.youtube.com/watch?v=U6Wvmrc3akc>

HOW PHOTODIODES WORK

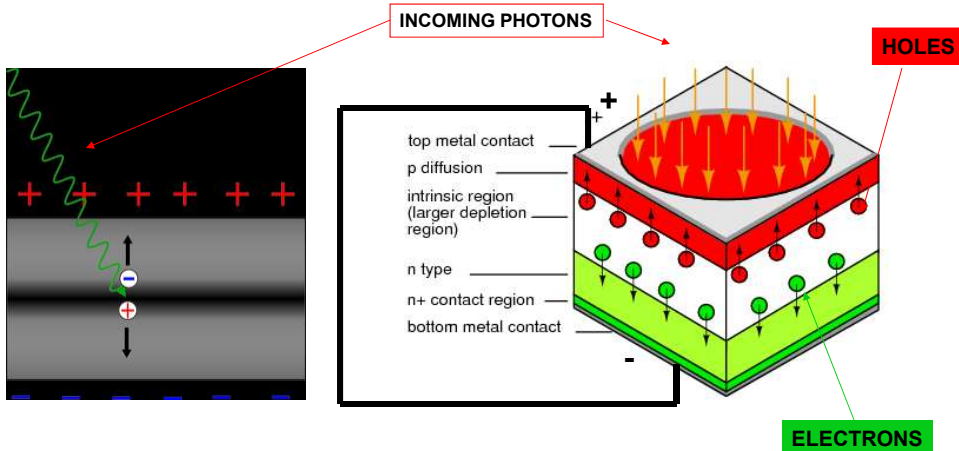
A INCOMING PHOTON WILL CREATE A HOLE ELECTRON PAIR AT THE PN JUNCTION. A CURRENT WILL FLOW IF BOTH SIDES ARE CONNECTED.





The Photodiode <http://www.youtube.com/watch?v=U6Wvmrc3akc>

TYPES OF PHOTODIODES

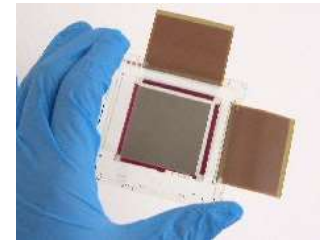
SMALL AREA PHOTODIODES
THESE HAVE VERY FAST RESPONSE TIMES



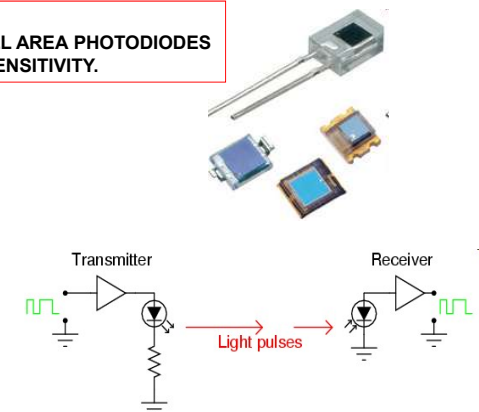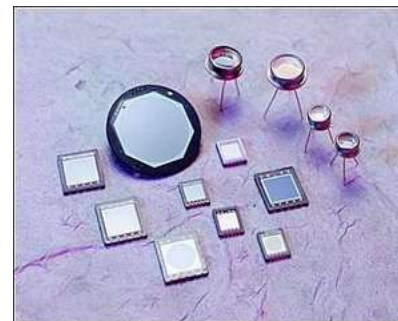
LARGE AREA PHOTODIODES
HAVE SLOWER RESPONSE TIMES THEN SMALL AREA PHOTODIODES
THESE LARGE SURFACE AREA GIVES HIGH SENSITIVITY.




COMPONENTS OF A PHOTODIODE

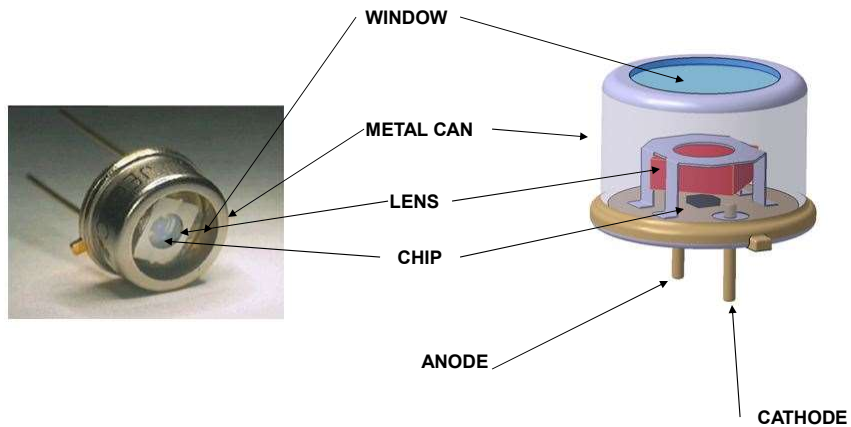


DIFFERENT PACKAGE STYLES FOR PHOTODIODES

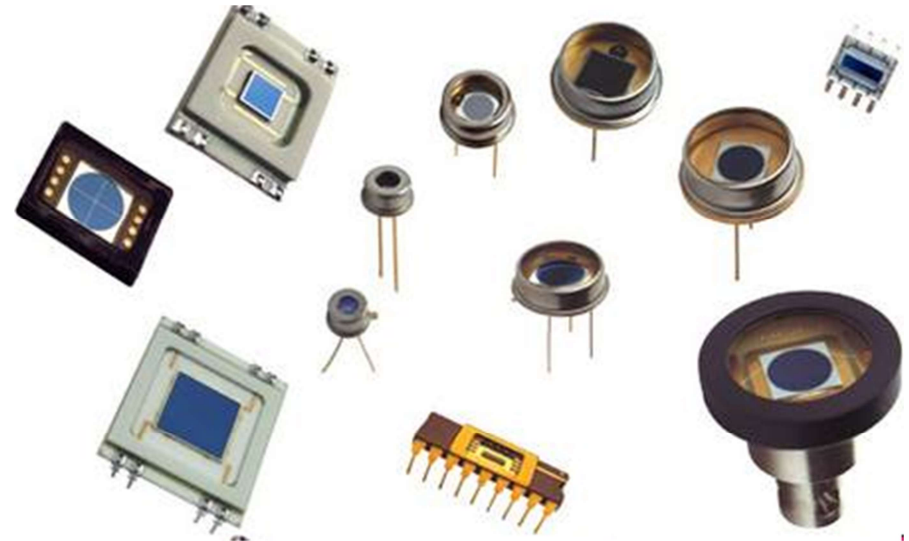


CHARGE COUPLED DEVICES (CCD)

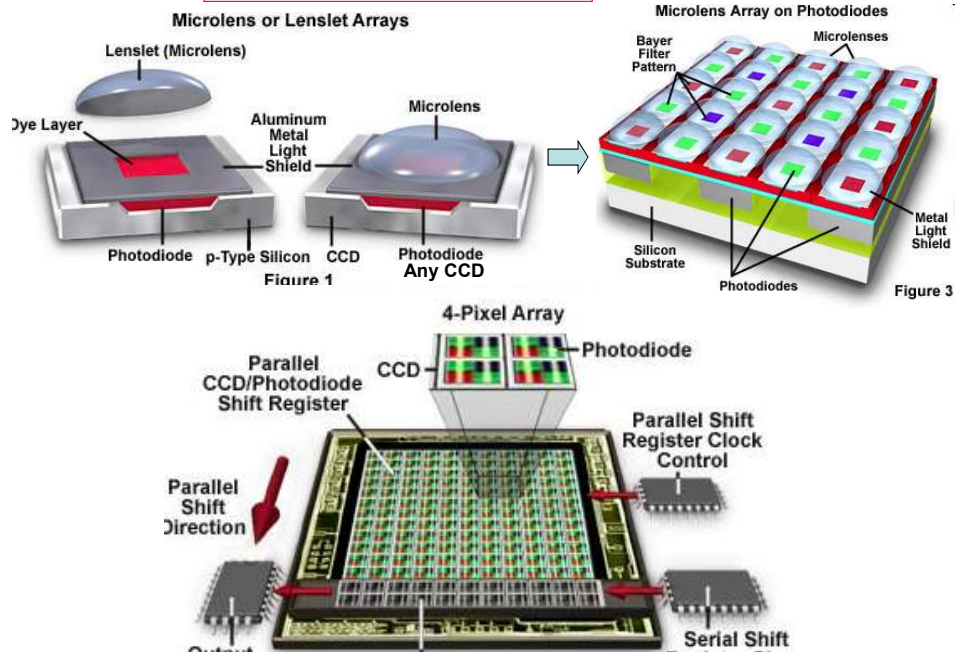

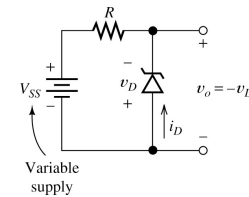Zener Diode - Voltage Regulator (reverse biased)



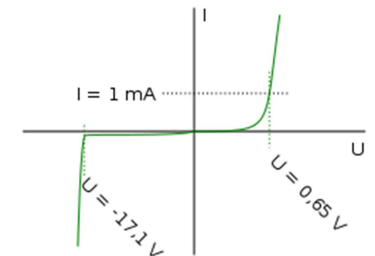
A simple regulator circuit that provides a nearly constant output voltage v_o from a variable supply voltage.



A **Zener diode** is a type of [diode](#) that permits [current](#) not only in the forward direction like a normal diode, but also in the reverse direction if the voltage is larger than the [breakdown voltage](#) known as "Zener knee voltage" or "Zener voltage".



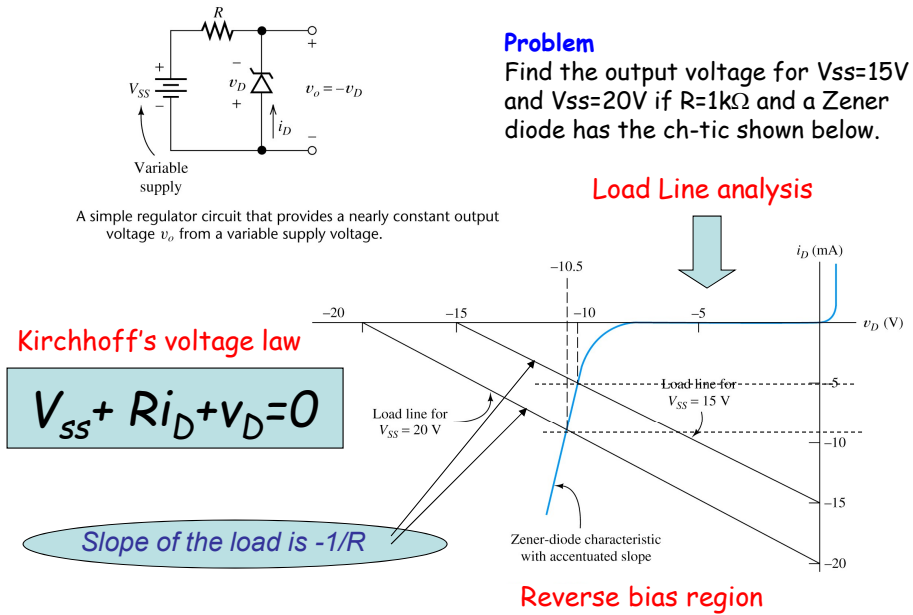Zener Diode - Voltage Regulator (reverse biased)



Load Line Analysis of Complex Circuits

Thevenin Equivalent

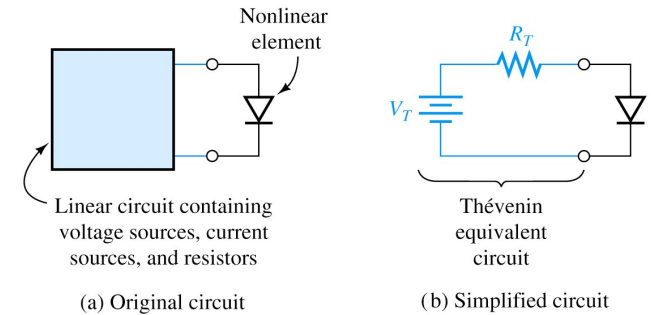


Figure 10.11 Analysis of a circuit containing a single nonlinear element can be accomplished by load-line analysis of a simplified circuit.

Voltage Regulator (1)

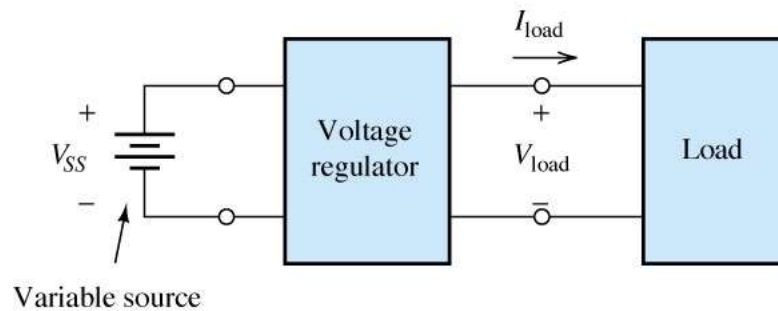


Figure 3.24 A voltage regulator supplies constant voltage to a load.

Voltage Regulator (2)


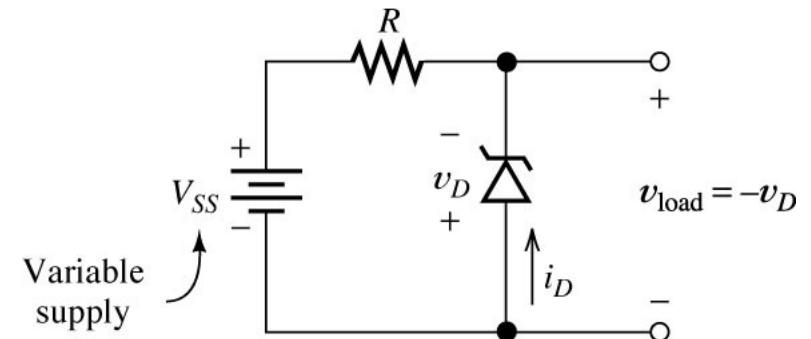


Figure 3.25 A simple regulator circuit that provides a nearly constant output voltage from a variable supply voltage.

Voltage Regulator (3)

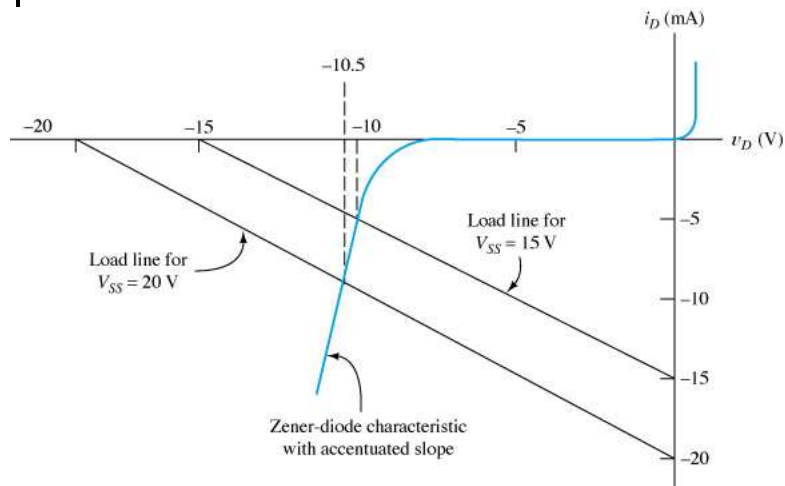

37

Designing a power supply


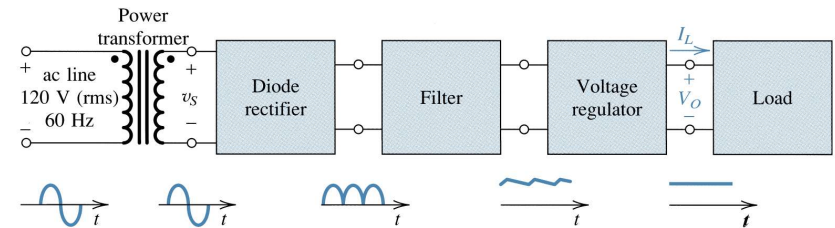


Fig. 3.36 Block diagram of a dc power supply.

38

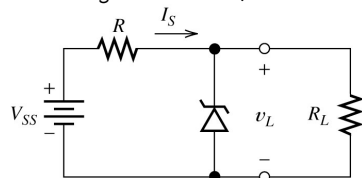Problem


Consider the Zener diode regulator shown in figure (a). Find the load voltage v_L and the source current i_S if $V_{SS}=24$ V, $R=1.2$ k Ω and $R_L=6$ k Ω .




(a) Regulator circuit with load

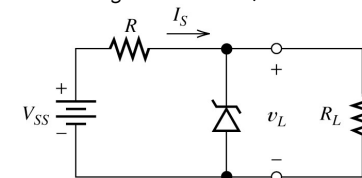Problem

Consider the Zener diode regulator shown in figure (a). Find the load voltage v_L and the source current i_S if $V_{SS}=24$ V, $R=1.2$ k Ω and $R_L=6$ k Ω .



(a) Regulator circuit with load

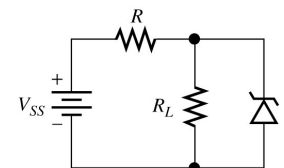


(b) Circuit of (a) redrawn

Exercise – find Thevenin equivalent

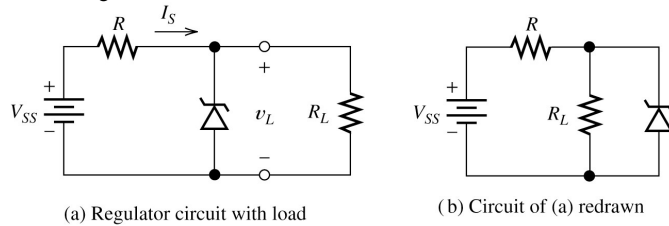Problem


Consider the Zener diode regulator shown in figure (a). Find the load voltage v_L and the source current i_S if $V_{SS}=24V$, $R=1.2k\Omega$ and $R_L=6k\Omega$.



Thevenin equivalent

$$V_T = V_{SS} * (R_L / (R + R_L)) = 20V$$

$$R_T = (R R_L) / (R + R_L) = 1k\Omega$$

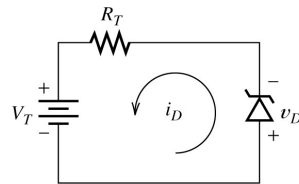

(c) Circuit with linear portion

Load line equation

$$V_T + R_T i_D + V_D = 0$$

$$V_L = -V_D = 10V$$

$$i_D = -10mA$$

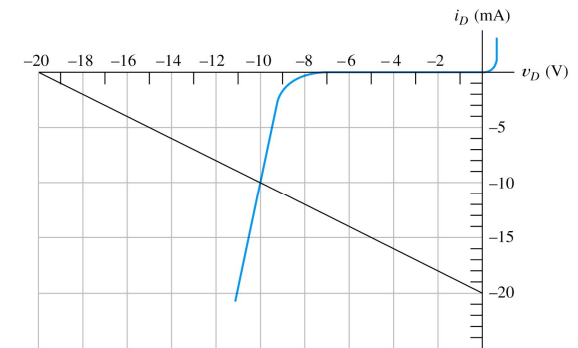


Figure 10.13 Zener-diode characteristic for Example 10.4 and Exercise 10.4.

Finally $i_S = (V_{SS} - V_L) / R = 11.67 \text{ mA}$ (from circuit "a")

Exercise 10.4 & 10.5

Ideal diode Model

Useful for circuits with more than one diode


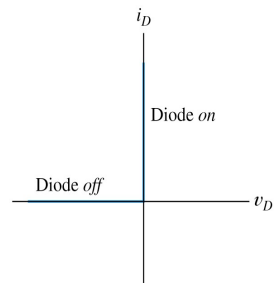


Figure 10.15 Ideal-diode volt-ampere characteristic.

- (1) Assume a state for each diode, either "on" or "off" - 2^n combinations
- (2) Assume a short circuit for diode "on" and an open circuit for diode "off"
- (3) Check to see if the result is consistent with the assumed state for each diode (current must flow in the forward direction for diode "on" and the voltage across the diodes assumed to be "off" must be positive at the cathode - reverse bias)
- (4) If the results are consistent with the assumed states, the analysis is finished. Otherwise return to step (1) and choose a different combination of diode states.

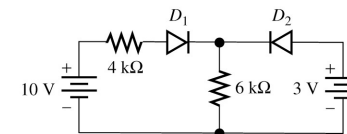Problem

Analyze the circuit shown below using the ideal diode model. Start by assuming the **D1 is off and D2 is on**.




(a) Circuit diagram


Exercise 10.6 & 10.7 & 10.8

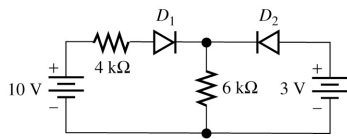Problem

Analyze the circuit shown below using the ideal diode model. Start by assuming the **D1 is off and D2 is on**.



(a) Circuit diagram

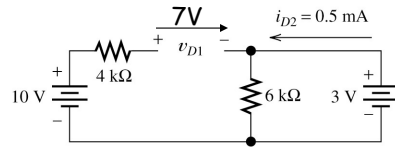


(b) Equivalent circuit assuming D_1 off and D_2 on (since $v_{D1} = +7\text{ V}$, this assumption is not correct)


Not consistent with the assumption that D_1 is off

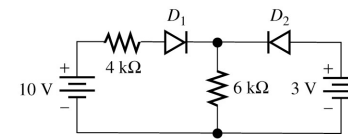Problem


Analyze the circuit shown below using the ideal diode model. Start by assuming the **D1 is off and D2 is on**.



(a) Circuit diagram

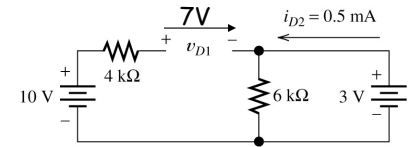

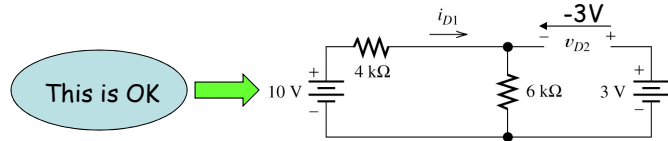(b) Equivalent circuit assuming D_1 off and D_2 on (since $v_{D1} = +7\text{ V}$, this assumption is not correct)



(c) Equivalent circuit assuming D_1 on and D_2 off (this is the correct assumption since i_{D1} turns out to be a positive value and v_{D2} turns out negative)

This is OK

Piecewise Linear Diode Models

More accurate than the ideal diode model and does not rely on nonlinear equation or graphical techniques.


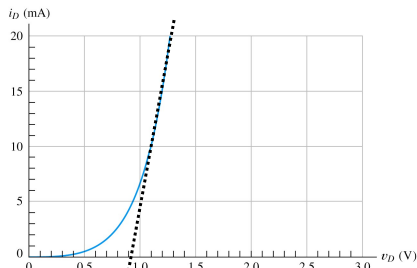


Figure 10.8 Diode characteristic for Exercise 10.3.

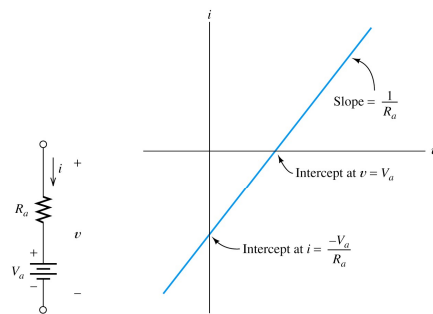- (1) Diode V-I characteristic approximated by straight line segments
- (2) We model each section of the diode I-V characteristic with R in series with a fixed voltage source



(a) Circuit diagram

(b) Volt-ampere characteristic

Figure 10.18 Circuit and volt-ampere characteristic for piecewise-linear models.

Problem

Find circuit models for the Zener-diode volt-ampere characteristic shown in figure below using the piecewise-linear diode model.

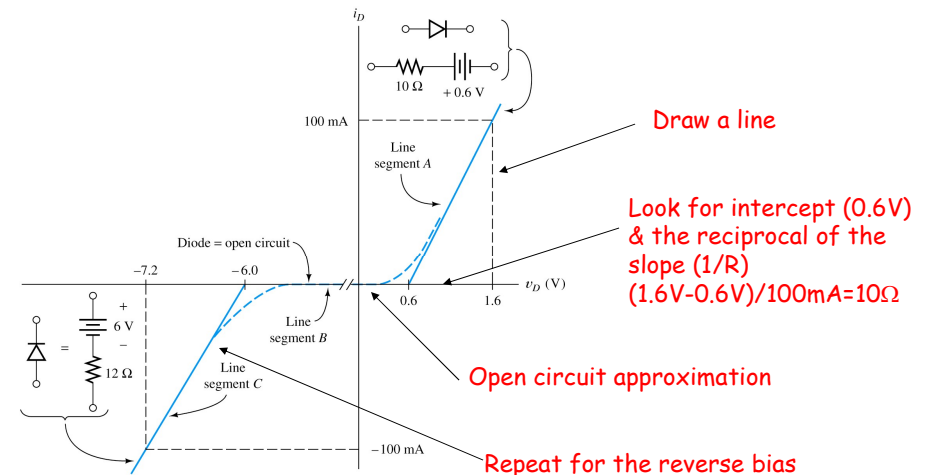


Figure 10.19 Piecewise-linear models for the diode of Example 10.6.

Exercise 10.7

HOW DIODES ARE USED



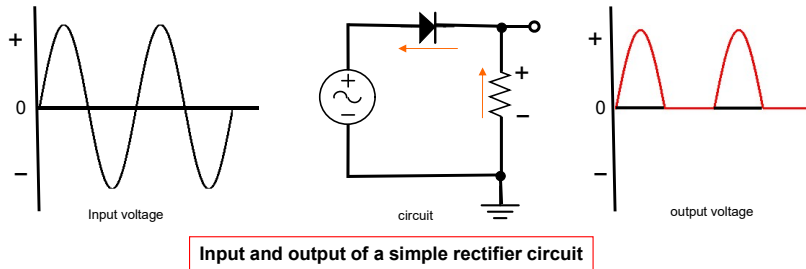
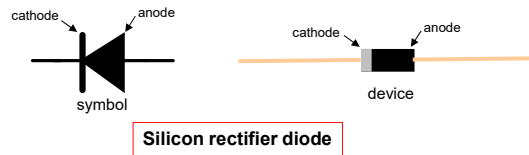


Fig. 8-23 p.219 A single-phase half-wave rectifier circuit produces one output pulse of dc for each cycle of ac input.


Power Diode Rectifier

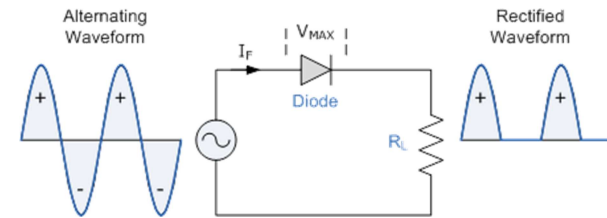


Half Wave Rectifier Circuit

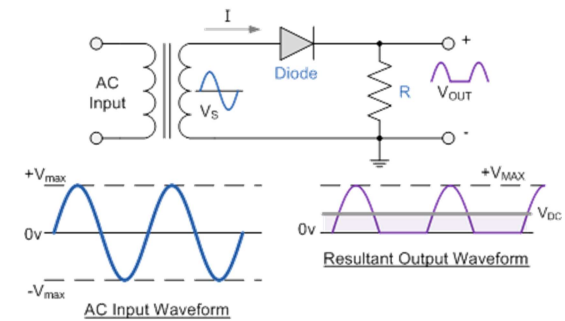

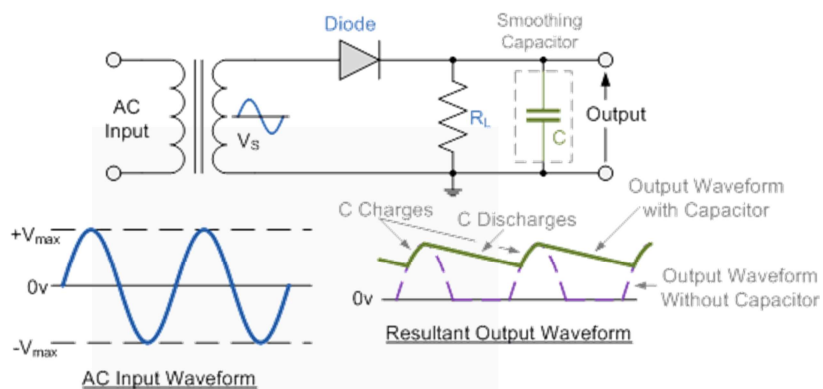
Half-wave Rectifier with Smoothing Capacitor




Full Wave Rectifier Circuit

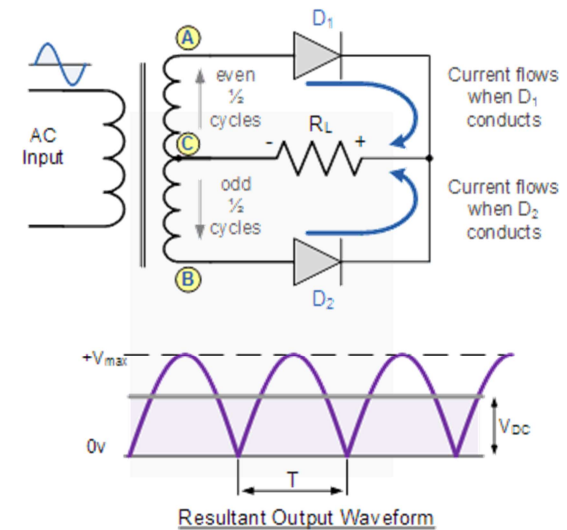


The Diode Bridge Rectifier

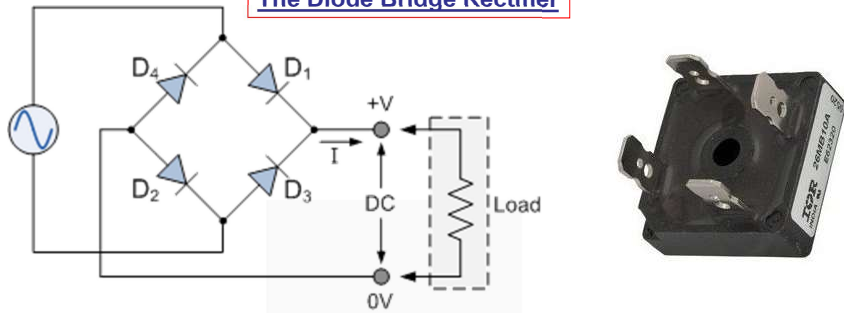


The Positive Half-cycle

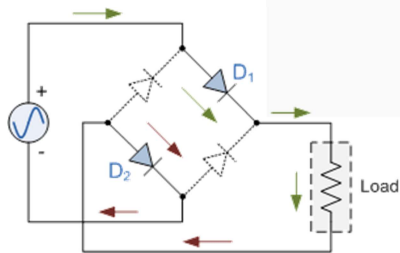

The Negative Half-cycle

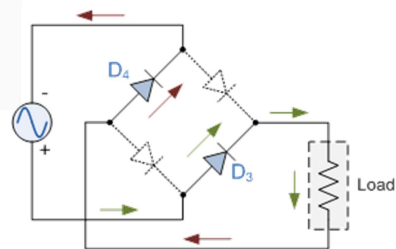


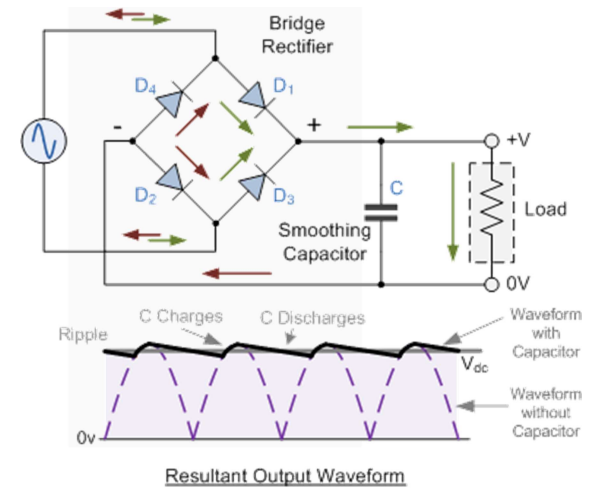
Full-wave Rectifier with Smoothing Capacitor



Full Wave Bridge Rectifier

<http://www.youtube.com/watch?v=aCfAdIRrw7M>

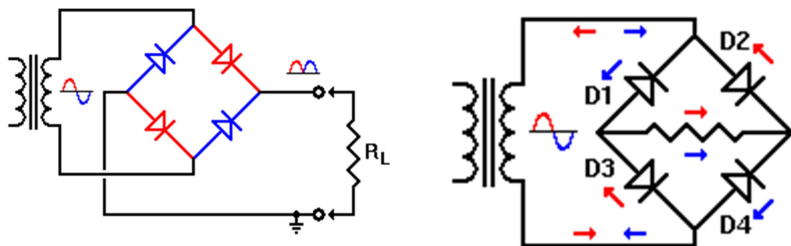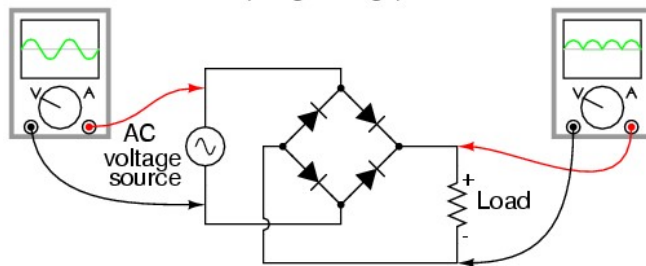Full-wave rectifier circuit (bridge design)



VARIOUS TYPES OF POWER RECTIFIERS



<https://www.youtube.com/watch?v=yk6VMBLrvM>

Various printed circuit board mounted rectifiers and voltage regulators

1N4001, 1N4002, 1N4003, 1N4004, 1N4005, 1N4006, 1N4007

Axial Lead Standard Recovery Rectifiers


This data sheet provides information on subminiature size, axial lead mounted rectifiers for general-purpose low-power applications.

Features

- Shipped in plastic bags, 1000 per bag
- Available Tape and Reel, 5000 per reel, by adding a "RL" suffix to the part number
- Available in Fan-Fold Packaging, 3000 per box, by adding a "FF" suffix to the part number
- Pb-Free Packages are Available

Mechanical Characteristics

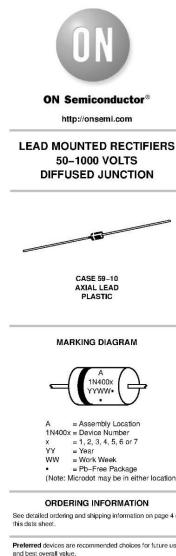- Case: Epoxy Moulded
- Weight: 0.4 gram (approximately)
- Finish: All External Surfaces Corrosion Resistant and Terminal Leads are Readily Solderable
- Lead and Mounting Surface Temperature for Soldering Purposes: 260°C Max. for 10 Seconds, 10/6 in. from case
- Polarity: Cathode Indicated by Polarity Band



*For additional information on our Pb-Free strategy and soldering details, please download the ON Semiconductor Soldering and Mounting Techniques Reference Manual, SOLDERRM.




1N4001 - 1N4007 1.0A RECTIFIER

Features

- Diffused Junction
- High Current Capability and Low Forward Voltage Drop
- Surge Overload Rating to 30A Peak
- Low Reverse Leakage Current
- Lead Free Finish, RoHS Compliant (Note 3)

Mechanical Data

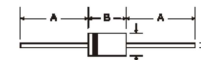- Case: DO-41
- Case Material: Molded Plastic, UL Flammability Classification Rating 94V-0
- Molded Lead: 1 per J-STD-020D
- Terminal: Finish - Bright Tin, Plated Leads Solderable per MIL-STD-202, Method 208
- Polarity: Cathode Band
- Mounting Position: Any
- Ordering Information: See Page 2
- Marking: Type Number
- Weight: 0.30 grams (approximate)



Dim	DO-41 Plastic	Min	Max
A	25.40	—	—
B	4.56	0.21	—
C	0.71	0.264	—
D	2.00	2.72	—
All Dimensions in mm			

XYYY
XN YYY

COMPONENT IDENTIFICATION NUMBER

X - NUMBER OF SEMICONDUCTOR JUNCTIONS
N - A SEMICONDUCTOR
YYY - IDENTIFICATION NUMBER (ORDER OR REGISTRATION NUMBER)
ALSO INCLUDES SUFFIX LETTER (IF APPLICABLE) TO INDICATE

- MATCHING DEVICES
- REVERSE POLARITY
- MODIFICATION

EXAMPLE - 1N454 (AN IMPROVED VERSION OF THE SEMICONDUCTOR CODE TYPE 345)

Maximum Ratings and Electrical Characteristics @T_A = 25°C unless otherwise specified

Single phase, half wave, 50/60 Hz, resistive or inductive load.
For capacitive load, derate current by 20%.

Characteristic	Symbol	1N4001	1N4002	1N4003	1N4004	1N4005	1N4006	1N4007	Unit
Peak Repetitive Reverse Voltage	V _{RRM}	50	100	200	400	600	800	1000	V
Working Peak Reverse Voltage	V _{WRM}	35	70	140	280	420	560	700	V
DC Blocking Voltage	V _{DRM}	35	70	140	280	420	560	700	V
Average Rectified Output Current (Note 1) @ T _A = 75°C	I _A	1.0							A
Non-Repetitive Peak Forward Surge Current (10ms single half sine-wave superimposed on rated load)	I _{FSM}	30							A
Forward Voltage @ I _A = 1.0A	V _{FM}	1.0							V
Peak Reverse Current @ T _A = 25°C at Rated DC Blocking Voltage @ T _A = 100°C	I _{RS}	5.0							µA
Typical Junction Capacitance (Note 2)	C _J	15							pF
Typical Thermal Resistance Junction to Ambient	R _{JA}	100							K/W
Maximum DC Blocking Voltage Temperature	T _A	+150							°C
Operating and Storage Temperature Range	T _A , T _{STG}	-55 to +150							°C

Notes:
1. Leads maintained at ambient temperature at a distance of 8.0mm from the case.
2. Measured at 1.0 MHz and applied reverse voltage of 4.0V DC.
3. EU Directive 2002/95/EC (RoHS). All applicable RoHS exemptions applied, see EU Directive 2002/95/EC Annex Tables.



1N 4001 ... 1N 4007, 1N 4007-1300
EM 513, EM 516, EM 518

Silicon Rectifiers	Silizium Gleichrichter
Nominal current – Nennstrom	1 A
Repetitive peak reverse voltage Periodische Spitzenspannung	50...2000 V
Plastic case Kunststoffgehäuse	DO-41 DO-204AL
Weight approx. – Gewicht ca.	0.4 g
Plastic material has UL classification 94V-0 Gehäusmaterial UL94V-0 klassifiziert	
Standard packaging taped in ammo pack Standard Lieferform gegurtet in Ammo-Pack	see page 16 siehe Seite 16

Maximum ratings	Grenzwerte
Type	Repetitive peak reverse voltage Periodische Spitzenspannung
Typ	V _{RRM} [V]
1N 4001	50
1N 4002	100
1N 4003	200
1N 4004	400
1N 4005	600
1N 4006	800
1N 4007	1000
1N 4007-1300	1300
EM 513	1600
EM 516	1800
EM 518	2000

Max. average forward rectified current, R-load Dauergrrenzstrom in Einwegschaltung mit R-Last	T _A = 75°C T _A = 100°C	I _{FAV} I _{FAV}	1 A) 0.75 A)
Repetitive peak forward current Periodischer Spitzenstrom	f > 15 Hz	I _{FRM}	10 A)
Peak forward surge current, 50 Hz half sine-wave Stoßstrom für eine 50 Hz Sinus-Halbwellen	T _A = 25°C	I _{FSM}	50 A

) Valid, if leads are kept at ambient temperature at a distance of 10 mm from case
Örtlich, wenn die Anschlußdrähte in 10 mm Abstand von Gehäuse auf Umgebungstemperatur gehalten werden

