
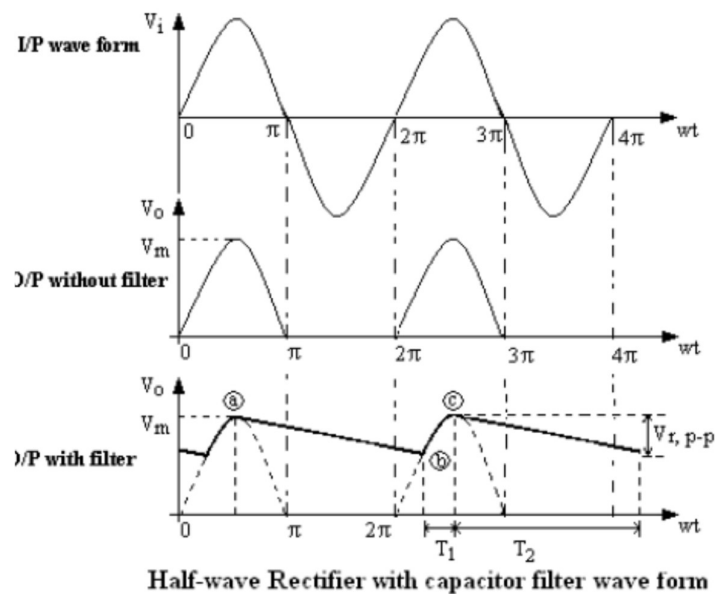
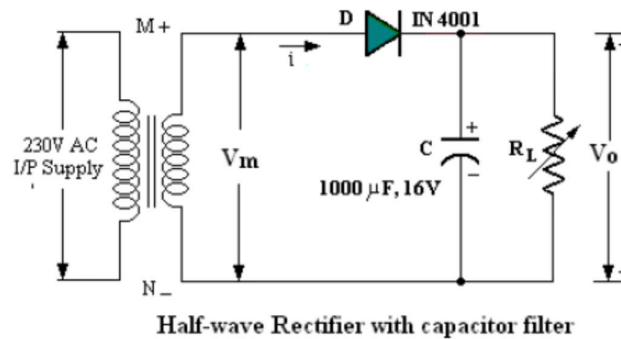


## การทดลองที่ 4 RECTIFIERS
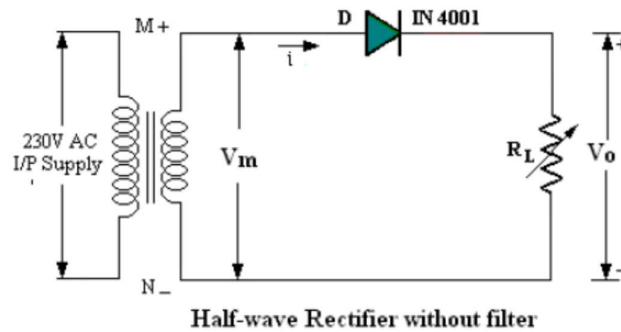
### 4.1 HALF-WAVE RECTIFIERS WITHOUT CAPACITOR FILTER AND WITH CAPACITOR FILTER:



#### WITHOUT FILTER:

1. Connecting the circuit on bread board as per the circuit diagram
2. Connect the primary of the transformer to main supply i.e. 230V, 50Hz
3. Connect the decade resistance box and set the  $R_L$  value to  $100\Omega$
4. Connect the Multimeter at output terminals and vary the load resistance (DRB)

from  $100\Omega$  to  $1K\Omega$  and note down the  $V_{ac}$  and  $V_{dc}$  as per given tabular form

5. Disconnect load resistance (DRB) and note down no load voltage  $V_{dc}$  ( $V_{no\ load}$ )

6. Connect load resistance at  $1K\Omega$  and connect Channel – II of Oscilloscope at output terminals and CH – I of OSCILLOSCOPE at Secondary Input terminals observe and note down the Input and Output Wave form on Graph Sheet.

7. Calculate ripple factor

$$\gamma = \frac{V_{ac}}{V_{dc}}$$

8. Calculate Percentage of Regulation,

$$\% \eta = \frac{V_{no\ load} - V_{full\ load}}{V_{no\ load}} * 100\%$$

V no load = \_\_\_\_\_  $V_{ac}$  \_\_\_\_\_  $V_{dc}$


S. No.	RL ( $\Omega$ )	O/P Voltage ( $V_o$ )		Ripple factor	% of Regulation
		$V_{ac}(V)$	$V_{dc}(V)$		
1	100				
2	200				
3	300				
4	400				
5	500				
6	600				
7	700				
8	800				
9	900				
10	1K				

#### WITH CAPACITOR FILTER:

1. Connecting the circuit as per the circuit Diagram and repeat the above procedure from steps 2 to 8.

V no load = \_\_\_\_\_  $V_{ac}$  \_\_\_\_\_  $V_{dc}$

S. No.	RL ( $\Omega$ )	O/P Voltage ( $V_o$ )		Ripple factor	% of Regulation
		$V_{ac}(V)$	$V_{dc}(V)$		
1	100				
2	200				
3	300				
4	400				
5	500				
6	600				
7	700				
8	800				
9	900				
10	1K				

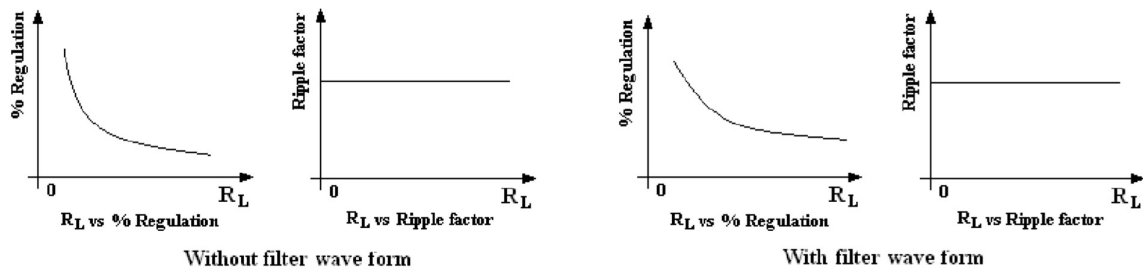**MODEL GRAPHS:**

**RESULT:** Observe Input and Output Wave forms and Calculate ripple factor and percentage of regulation in Half wave rectifier with and without filter.

Drawn Input and Output Wave forms

**Without Filter:**

Ripple Factor:

Regulation:


**With Capacitor Filter:**

Ripple Factor:


Regulation:

**PRECAUTIONS:**


1. Check the wires for continuity before use.
2. Keep the power supply at Zero volts before Start.
3. All the contacts must be intact.

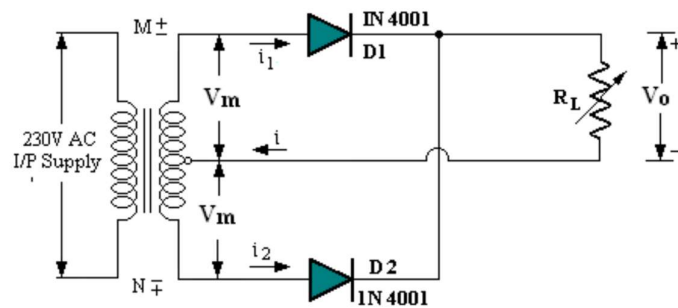**4.2 FULL-WAVE RECTIFIERS**

Full-wave Rectifier without filter

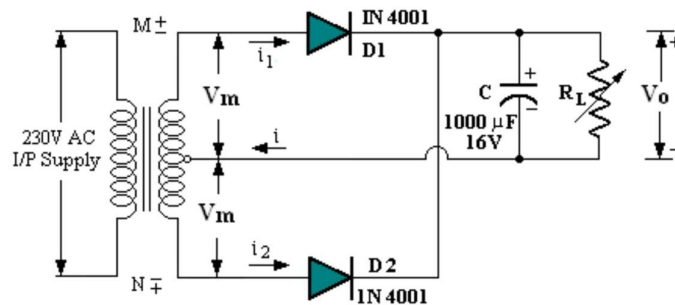

Full-wave Rectifier with capacitor filter

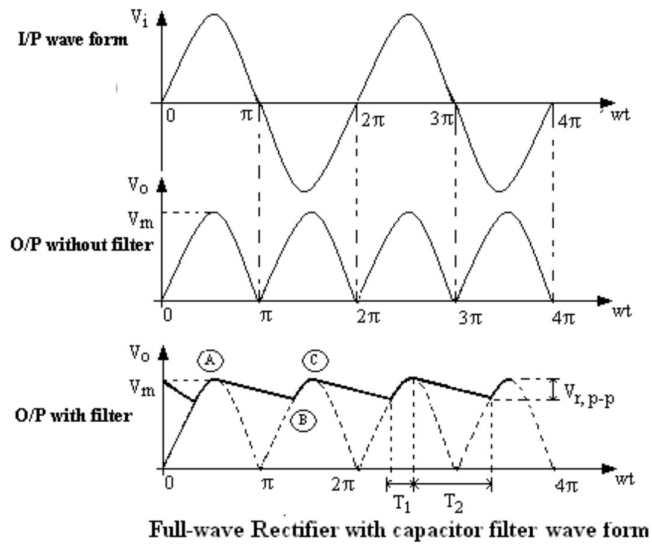**WITHOUT FILTER:**

V no load = \_\_\_\_\_  $V_{ac}$  \_\_\_\_\_  $V_{dc}$

S. No.	RL ( $\Omega$ )	O/P Voltage ( $V_o$ ) $V_{ac}(V)$ $V_{dc}(V)$		Ripple factor	% of Regulation
1	100				
2	200				
3	300				
4	400				
5	500				
6	600				
7	700				
8	800				
9	900				
10	1K				

**WITH CAPACITOR FILTER:**

V no load = \_\_\_\_\_  $V_{ac}$  \_\_\_\_\_  $V_{dc}$

S. No.	RL ( $\Omega$ )	O/P Voltage ( $V_o$ ) $V_{ac}(V)$ $V_{dc}(V)$		Ripple factor	% of Regulation
1	100				
2	200				
3	300				
4	400				
5	500				
6	600				
7	700				
8	800				
9	900				
10	1K				

**RESULT:** Observe Input and Output Wave forms and Calculate ripple factor and percentage of regulation in Half wave rectifier with and without filter.

**Without Filter:**

Ripple Factor:

Regulation:

**With Capacitor Filter:**


Ripple Factor:

Regulation:


**VIVA QUESTIONS:**

1. What is a rectifier?
2. How Diode acts as a rectifier?
3. What is the significance of PIV? What is the condition imposed on PIV?
4. Draw the o/p wave form without filter?
5. Draw the o/p wave form with filter?
6. What is meant by ripple factor? For a good filter whether ripple factor should be high or low?
7. What is meant by regulation?
6. What is meant by time constant?
8. What happens to the o/p wave form if we increase the capacitor value?
9. What happens if we decrease the capacitor value?


### 4.3 BRIDGE RECTIFIER

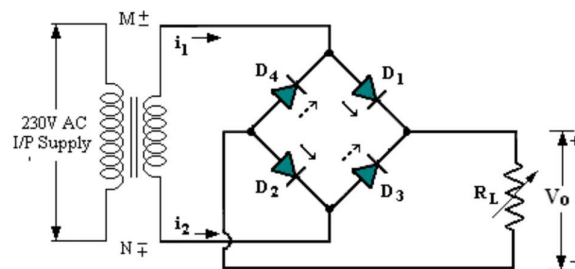

Bridge Rectifier without filter

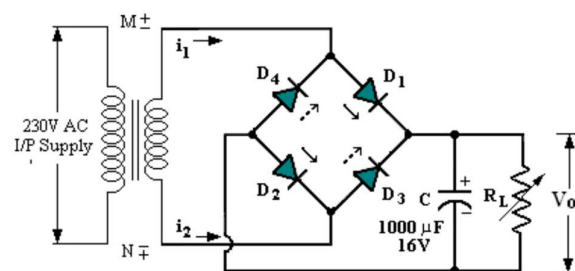

Bridge Rectifier with capacitor filter

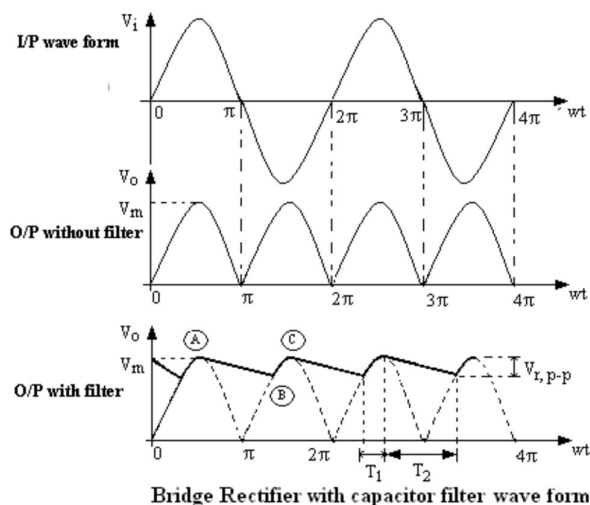**WITHOUT FILTER:**

V no load = \_\_\_\_\_ V<sub>ac</sub> \_\_\_\_\_ V<sub>dc</sub>

S. No.	RL (Ω)	O/P Voltage (V <sub>o</sub> )		Ripple factor	% of Regulation
		V <sub>ac</sub> (V)	V <sub>dc</sub> (V)		
1	100				
2	200				
3	300				
4	400				
5	500				
6	600				
7	700				
8	800				
9	900				
10	1K				

**WITH CAPACITOR FILTER:**

V no load = \_\_\_\_\_ V<sub>ac</sub> \_\_\_\_\_ V<sub>dc</sub>

S. No.	RL (Ω)	O/P Voltage (V <sub>o</sub> )		Ripple factor	% of Regulation
		V <sub>ac</sub> (V)	V <sub>dc</sub> (V)		
1	100				
2	200				
3	300				
4	400				
5	500				
6	600				
7	700				
8	800				
9	900				
10	1K				

